

# EN 304- ELECTRICAL ENERGY SYSTEMS



Department of Energy Science and Engineering

This is only reading material (not lecture slides)

Cl: Zakir H Rather

**Note:** Some contents of the reading material presented in the supporting slides are gleaned from different resources for which the copyright is retained by the respective owner/holder/creator/publisher. The instructor of EN 209 does not hold any copyrights to the material obtained from such various resources. You are advised to treat the supporting slides as education material and not to exchange, disseminate, or share them with any other entity.



## SLIDE DECK 5: TRANSFORMER



# Transformer- Definition



- A transformer is a static machine used for transforming power through electromagnetic induction from one circuit at a given voltage level to another circuit at different or same voltage level, however without changing frequency.
- It essentially consists of two windings, the primary and secondary, wound on a common laminated magnetic core.
- Transformers have no moving parts, rugged and durable in construction, thus requiring less maintenances. Therefore, they have a very high efficiency—as high as 99%.
- There is no electrical connection between the primary and secondary. Hence, the ac power is transferred from primary to secondary through magnetic flux

# Terminology



- $V_1$  = Applied ac voltage
- $V_2$  = Voltage across the load
- $E_1$  = Primary induced emf
- $E_2$  = Secondary induced emf
- $N_1$  = No of turns on the primary
- $N_2$  = No of turns on the secondary
- $I_1$  = current flowing in the primary
- $I_2$  = current flowing in the secondary

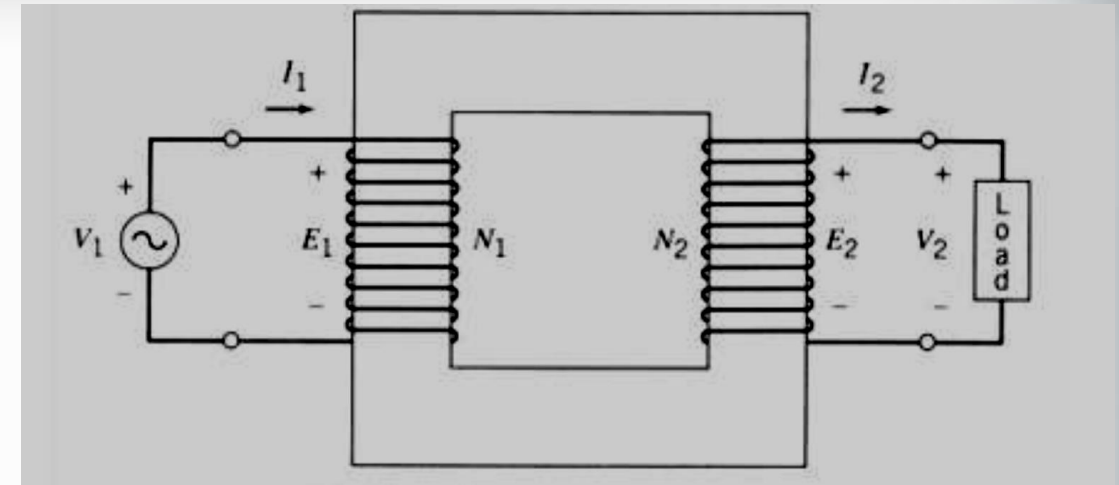


Fig 1: Two winding transformer

# Transformer: Principle of operation



- Transformers are devices that transfer energy from one circuit to another by means of a common magnetic field. Except auto-transformers, there is no direct electrical connection from one circuit to the other.
- Transformers work on the principle of electromagnetic induction, where mutual induction results in emf induced in the secondary winding.
- The ability of iron or steel to carry magnetic flux is much greater than air. Modern electrical steels have permeabilities in the order of 1500 compared with 1.0 for air. This means that the ability of a steel core to carry magnetic flux is 1500 times that of air.
- Ideally the flux generated by the first coil will be transferred through the transformer core, this flux induces an emf in the second coil and the voltage appears on the second winding terminals. Increasing the flux in the core requires increasing either the first coil voltage or number of turns. Increasing the second coil voltage for the same flux can be done by increasing the coil number of turns of the second coil.



# Transformer: Principle of operation



- There is no electrical connection between the primary and secondary. Hence, the a.c. power is transferred from primary to secondary through magnetic flux.
- Where,  $V_1$  = Applied a.c voltage,  $V_2$  = voltage across the load  
 $E_1$  = primary induced emf,  $E_2$  = Secondary induced emf  
 $N_1$  = No of turns on the primary,  $N_2$  = No of turns on the secondary  
 $I_1$  = current flowing in the primary,  $I_2$  = current flowing in the secondary
- If  $V_2 > V_1$ , it is called a **step up-transformer**. On the other hand, if  $V_2 < V_1$ , it is called a **step-down transformer**.
- **Working:** It works on the principle of **Faraday's laws of electromagnetic induction**

$$E_1 = -N_1 \frac{d\phi}{dt}, \quad E_2 = -N_2 \frac{d\phi}{dt} \quad \longrightarrow \quad \frac{E_2}{E_1} = \frac{N_2}{N_1}$$

# Ideal Transformer on No-Load:

An ideal transformer is one that has

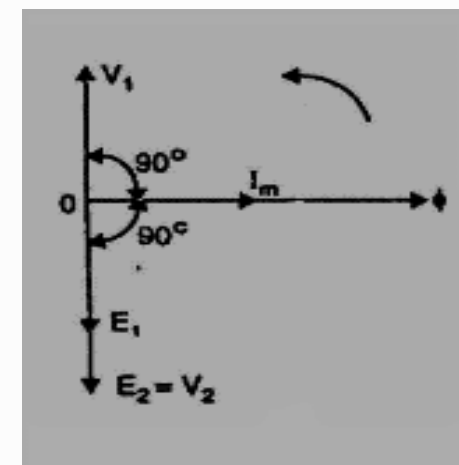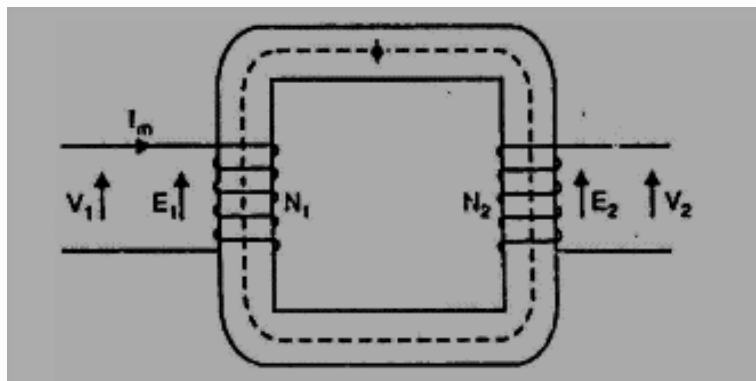1. **Zero leakage flux:** Fluxes produced by the primary and secondary currents are confined within the core
2. **The windings have no resistance:** Induced voltages equal to applied voltages
3. **The core has infinite permeability:** Reluctance (opposition to flux) of the core is zero;  
Negligible current is required to establish magnetic flux
4. **Loss-less magnetic core:** No hysteresis or eddy current losses



**Note:**  $V_1$  - supply voltage ;  $I_m$  - magnetising current;  $E_1$  - self induced emf ;  $E_2$  - mutually induced emf

# EMF Equation of a Transformer

The sinusoidal flux produced by the primary is  $\phi = \phi_m \sin \omega t$

The instantaneous emf induced in the primary is,  $e_1 = -N_1 \frac{d\phi}{dt} = -N_1 \frac{d}{dt}(\phi_m \sin \omega t) = -\omega \phi_m N_1 \cos \omega t$

$$e_1 = 2\pi f \phi_m N_1 \sin(\omega t - 90^\circ)$$

maximum value of induced emf,  $E_{m1} = 2\pi f \phi_m N_1$

The rms value is given by,  $E_1 = \frac{E_{m1}}{\sqrt{2}} = 4.44 f N_1 \phi_m$  ; Similarly  $E_2 = \frac{E_{m2}}{\sqrt{2}} = 4.44 f N_2 \phi_m$

In an ideal transformer,  $E_1 = V_1$  and  $E_2 = V_2$

volt-amperes input to the primary is equal to the output volt-amperes i.e.  $V_1 I_1 = V_2 I_2$

Voltage Transformation Ratio (K):


$$\frac{E_2}{E_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2} = K \quad \longrightarrow \quad \frac{V_1}{V_2} = \frac{I_2}{I_1} = \frac{N_1}{N_2}$$

# Ideal Transformer on Load:

- The secondary current  $I_2$  sets up an mmf  $N_2 I_2$  which produces a flux in the opposite direction to the flux  $\phi$  originally set up in the primary by the magnetizing current.
- power factor on the primary side is equal to the power factor on the secondary side


$$\phi_1 = \phi_2 \longrightarrow \cos \phi_1 = \cos \phi_2$$

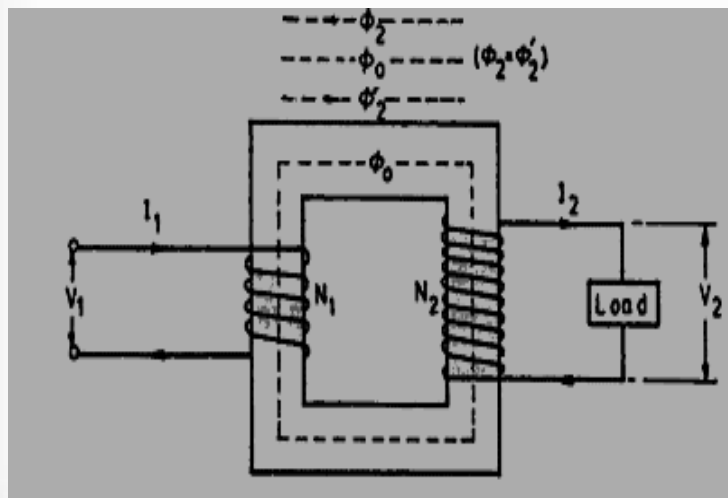- Since there are no losses in an ideal transformer, input primary power is equal to the secondary output power i.e.,  $V_1 I_1 \cos \phi_1 = V_2 I_2 \cos \phi_2$



$$N_1 I_1 = N_2 I_2$$

$$I_1 = \frac{N_2}{N_1} I_2 = k I_2$$

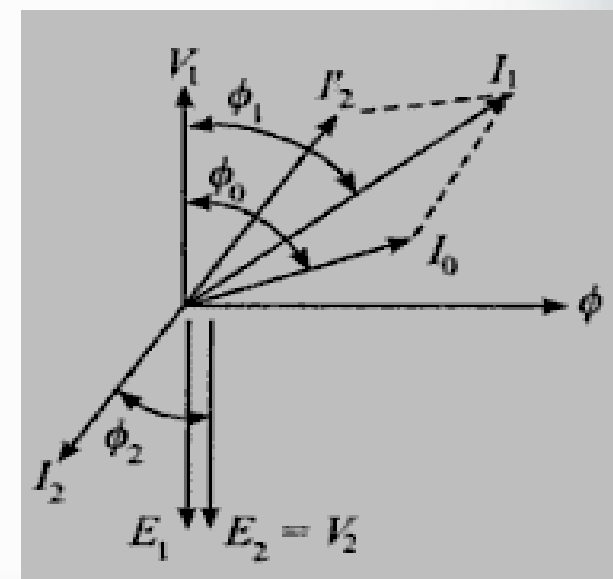




# Practical Transformer on No-Load:

A practical transformer differs from the ideal transformer in many respects. The practical transformer has

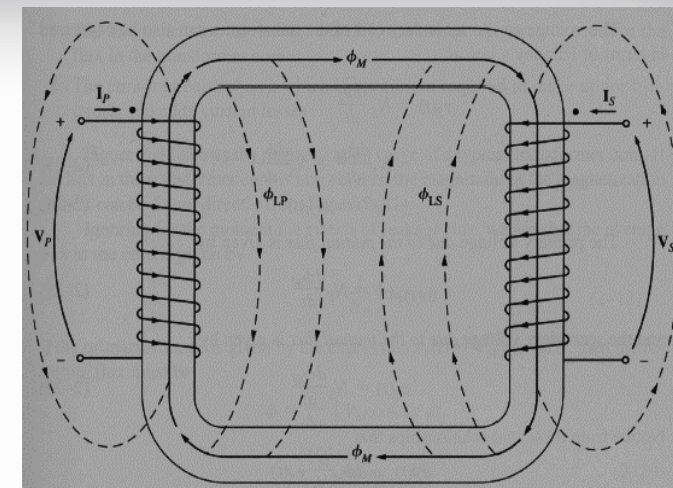- (i) iron losses
- (ii) winding resistances and
- (iii) magnetic leakage, giving rise to leakage reactances.



**Leakage flux:** flux that links only one of the transformer windings but not the other one

**Mutual flux:** flux that remains in the core and links both the windings

$\phi_p$ : total average primary flux

$\phi_M$ : flux linking both primary and secondary windings

$\phi_{LP}$ : primary leakage flux



$\phi_s$ : total average secondary flux

$\phi_{LS}$ : secondary leakage flux

$$\phi_P = \phi_M + \phi_{LP}$$

$$\phi_S = \phi_M + \phi_{LS}$$

# Practical Transformer on No-Load:

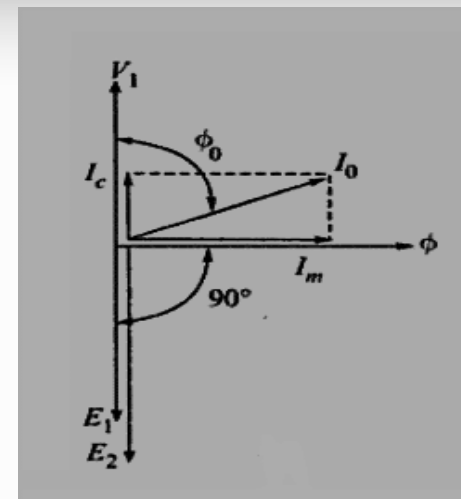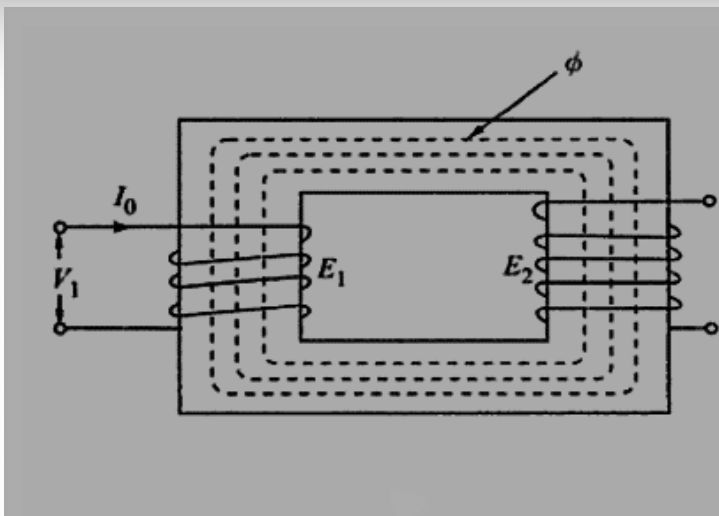

When an ac power source is connected to a transformer, a current flows in its primary circuit, even when the secondary circuit is open circuited. This current is the current required to produce flux in the ferromagnetic core and is called *excitation current*. It consists of two components:

1. The *magnetization current*  $I_m$ , which is the current required to produce the flux in the transformer core
2. The *core-loss current*  $I_c$ , which is the current required to make up for hysteresis and eddy current losses

# Practical Transformer on No-Load:

- The no-load primary current  $I_0$  can be resolved into two rectangular components:

$$I_c = I_0 \cos \phi_0 \text{ and } I_m = I_0 \sin \phi_0$$

$$I_0 = \sqrt{I_c^2 + I_m^2} \text{ and no load pf} = \cos \phi_0 = \frac{I_c}{I_0}$$


- It is to be known that no load primary copper loss (i.e.  $I_0^2 R$ ) is very small and may be neglected. Therefore, the no load primary input power is practically equal to the iron loss in the transformer i.e., No load input power,  $W_0 = \text{Iron loss}$

# Practical Transformer on Load:

## (1) No winding resistance and leakage flux -

The total primary current  $I_1$  must meet two requirements:

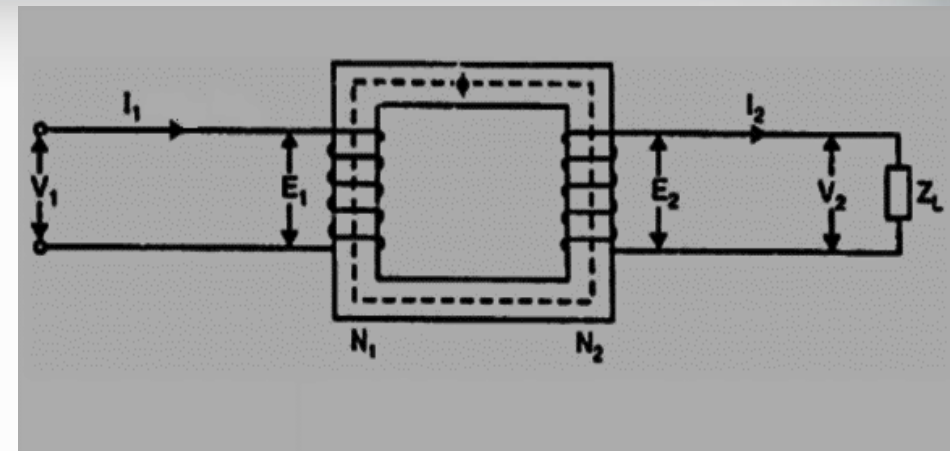- (a) It must supply the no-load current  $I_0$  to meet the iron losses in the transformer and to provide flux in the core.
- (b) It must supply a current  $I_0$  to counteract the demagnetizing effect of secondary current  $I_2$ .



The magnitude of  $I_2'$  will be such that:


$$N_1 I_2' = N_2 I_2$$

$$I_2' = \frac{N_2}{N_1} I_2 = K I_2$$

The total primary current  $I_1$  is the phasor sum of  $I_2'$  and  $I_0$ ;

$$I_1 = I_2' + I_0$$


$$I_2' = -K I_2$$

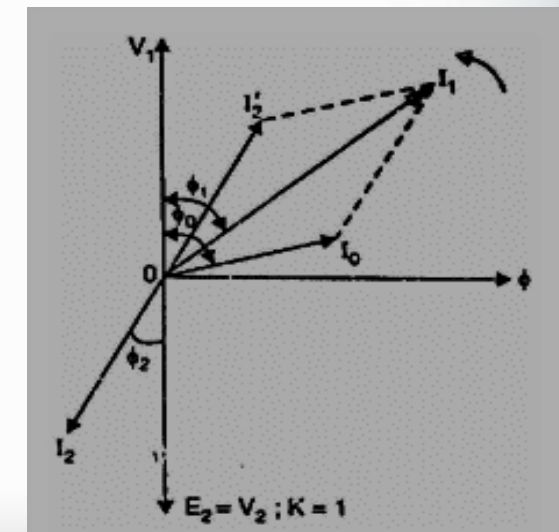

# Practical Transformer on Load:


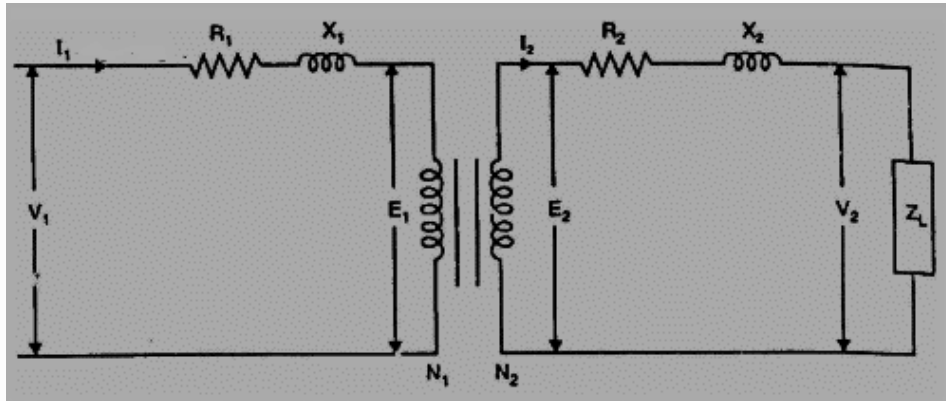
## (2) Transformer with resistance and leakage reactance:




The total primary current  $I_1$  is the phasor sum of  $I'_2$  and  $I_0$  ;

$$I_1 = I'_2 + I_0 \quad I_1 = I_0 + (-KI_2)$$

$$I'_2 = -KI_2$$
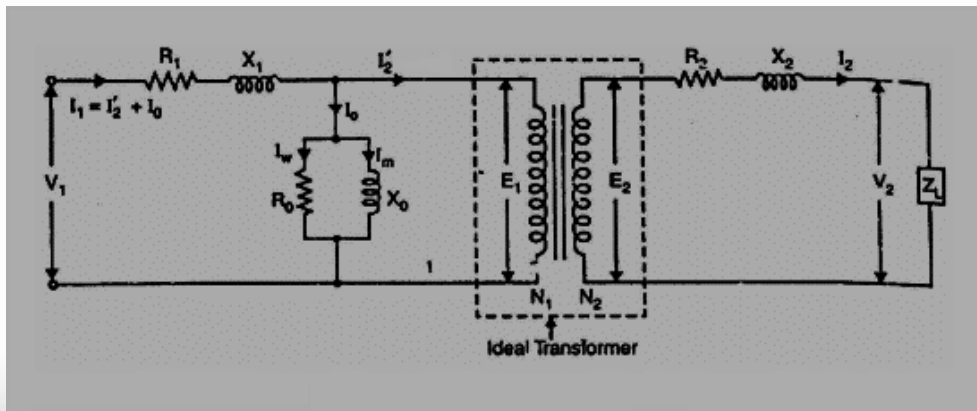
## (a) Exact Equivalent Circuit of a Loaded Transformer



$$\frac{E_2}{E_1} = \frac{N_2}{N_1} = \frac{I'_2}{I_2}$$

$$V_2 = E_2 - I_2(R_2 + jX_2) = E_2 - I_2 Z_2$$


$$V_1 = -E_1 + I_1(R_1 + jX_1) = -E_1 + I_1 Z_1$$




# Practical Transformer on Load contd..



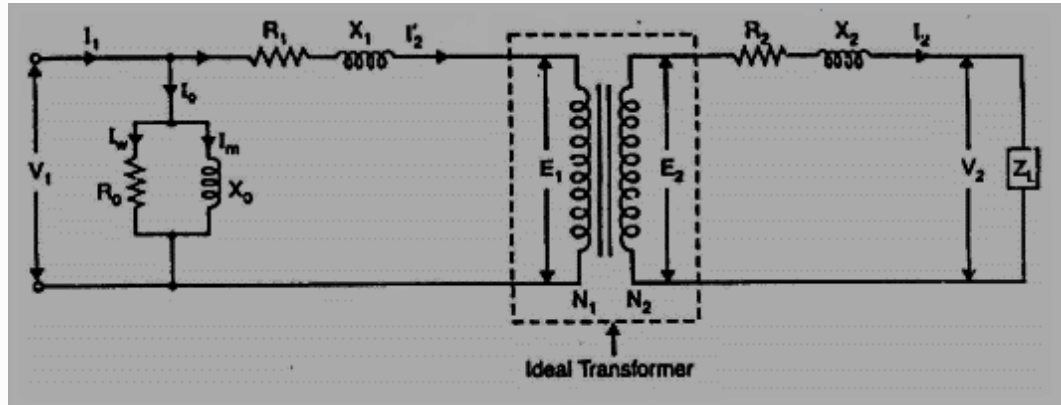
## (b) Approximate Equivalent Circuit of a Loaded Transformer



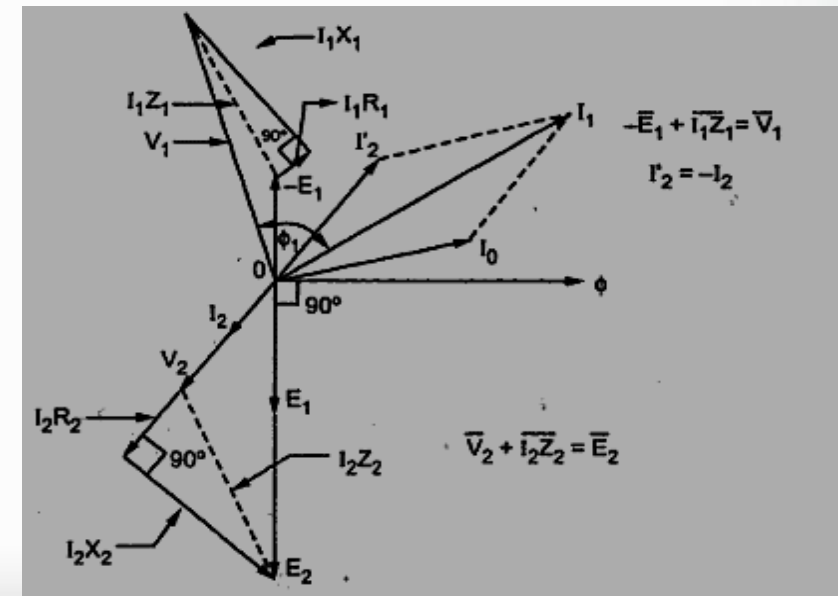
Phasor diagram for unity power factor load


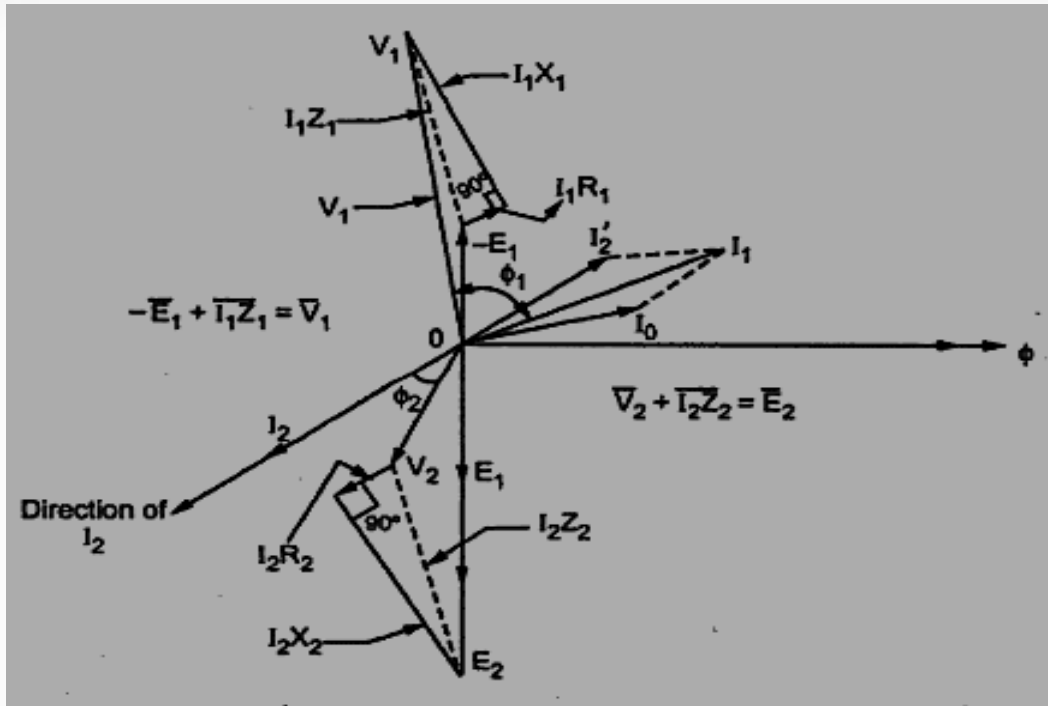
# Phasor diagrams for transformers on load



lagging power factor load

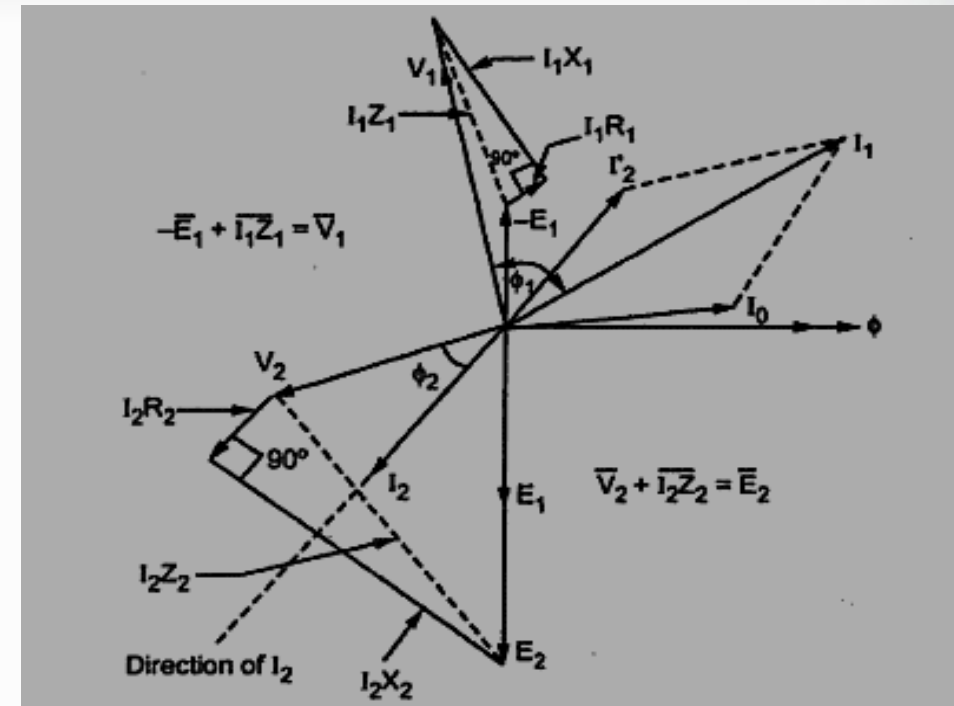

leading power factor load


# Equivalent Circuit of Transformer



The deviations from the ideal transformer are modelled in the equivalent circuit as follows:

- i. **Leakage flux** : Leakage flux is modelled as a leakage inductor in series, on both primary and secondary sides  $\longrightarrow X_{l1}, X_{l2}$
- ii. **Winding resistance**: Winding resistance of primary and secondary are both represented by resistors in series, on both primary and secondary sides  $\longrightarrow R_1, R_2$
- iii. **Finite permeability**(finite magnetizing current): A part of the input current goes as magnetizing current which is accounted by means of a shunt branch connected magnetizing inductor  $\longrightarrow X_m$
- iv. **Core losses**: Core losses are constant. It varies only with  $E_1^2$  or  $\Phi_m^2 f^2$ . It is represented by a shunt branch resistor  $\longrightarrow R_c$

# Equivalent Circuit of Transformer

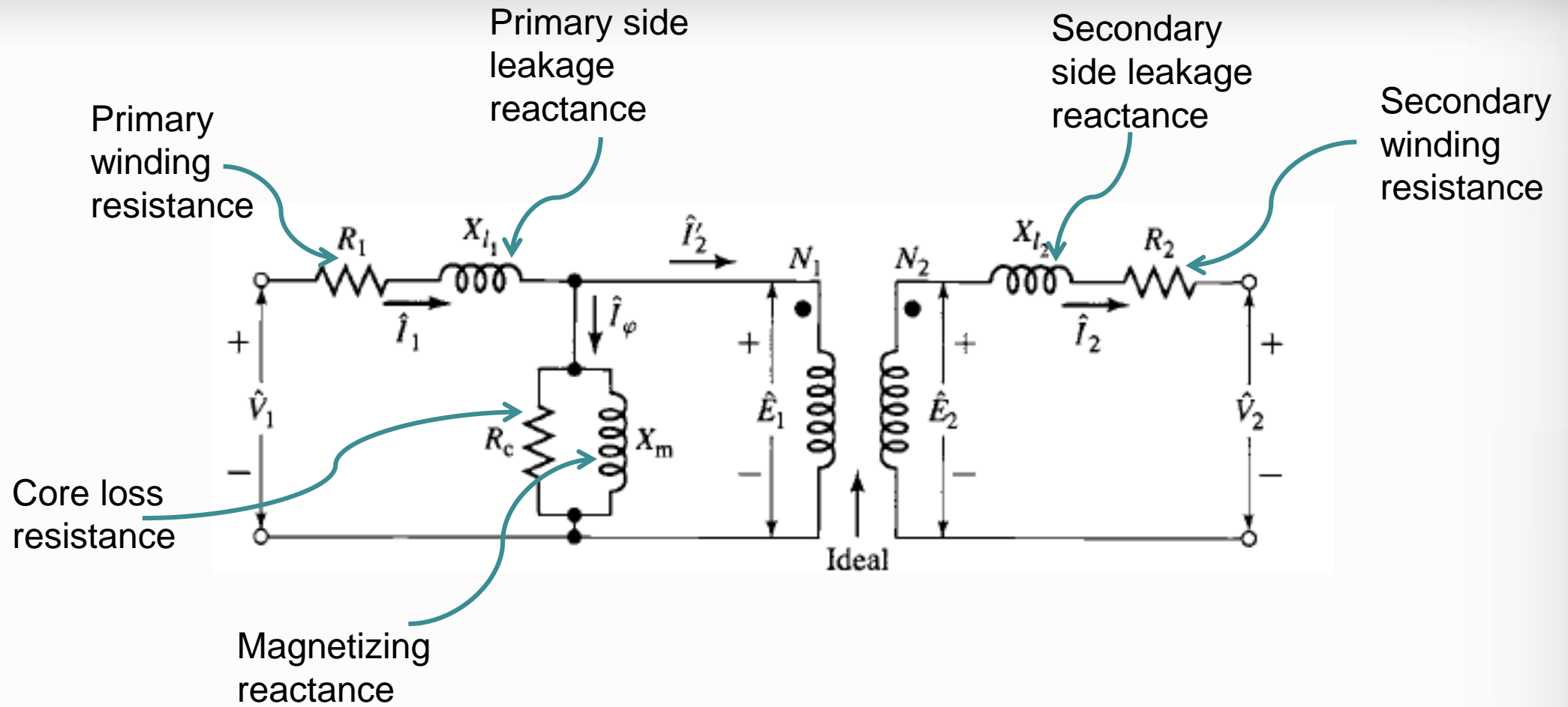

# Equivalent Circuit of Transformer

## ➤ Referring impedance on secondary side to primary side:

We know that  $Z_2$  on the secondary side is given by :  $Z_2 = \frac{V_2}{I_2}$

Now,  $Z_2$  can be written as follows:  $Z_2 = \frac{(N_2 / N_1) V_1}{(N_1 / N_2) I_1}$

The impedance measured across primary winding is  $Z_2' = \frac{V_1}{I_1} = \left( \frac{N_1}{N_2} \right)^2 Z_2$

Transformer ratio is given by:  $K = \frac{N_2}{N_1} = \frac{V_2}{V_1} = \frac{I_1}{I_2}$

Therefore, the impedance on secondary side **referred to primary** is given by  $Z_2' = \frac{1}{K^2} Z_2$


Similarly, when primary impedance is **referred to secondary** side, we get  $Z_1' = K^2 Z_1$




# Exact and Approximate Equivalent circuits



Exact Equivalent circuit:

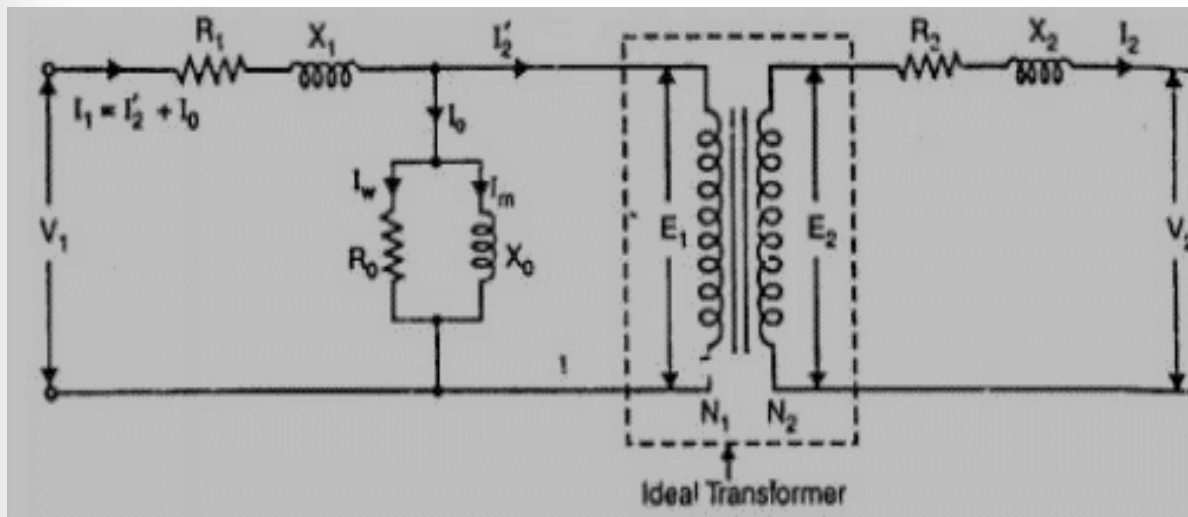


Approximate Equivalent circuit:

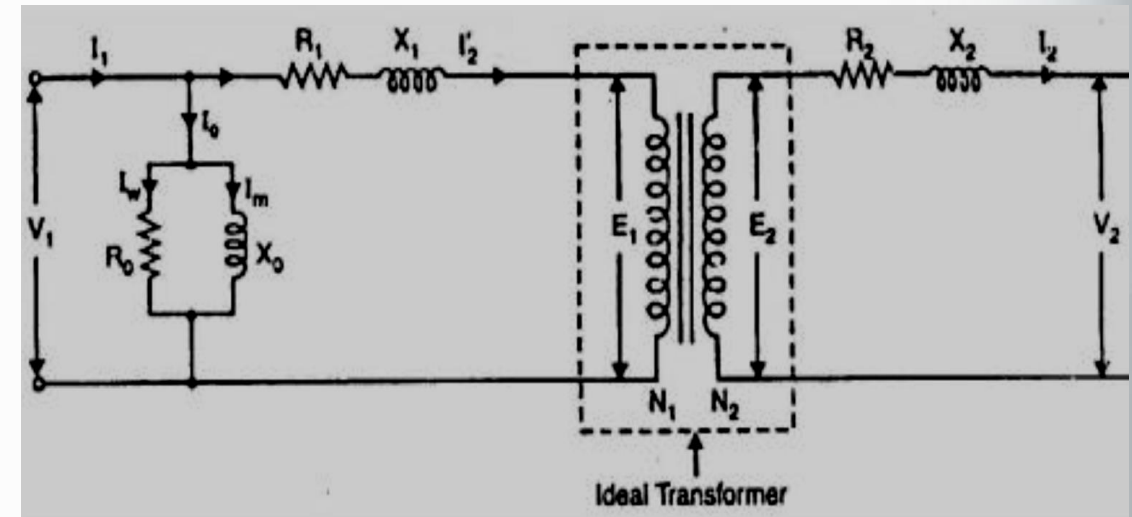

# Exact and Approximate Equivalent circuits referred to primary side
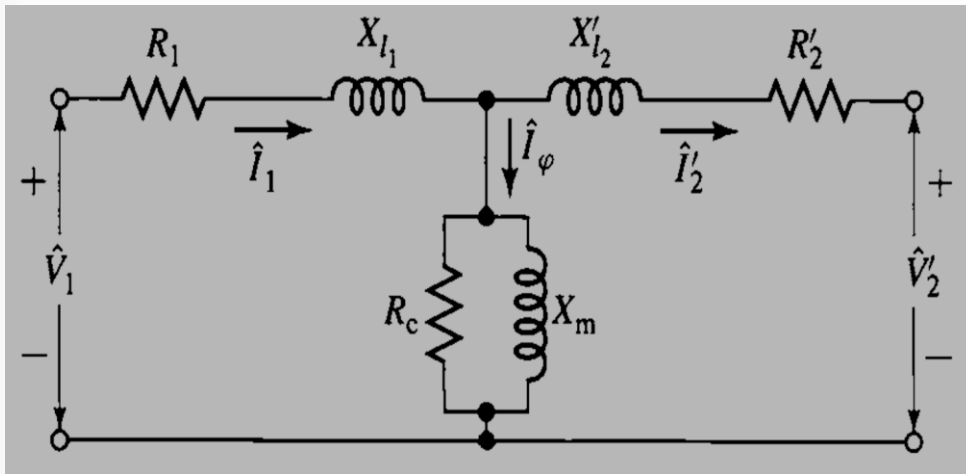
## Exact Equivalent circuit referred to primary side:




$$R_2' = R_2 / K^2$$

$$X_2' = X_2 / K^2$$

$$V_2' = V_2 / K$$

$$I_2' = KI_2$$
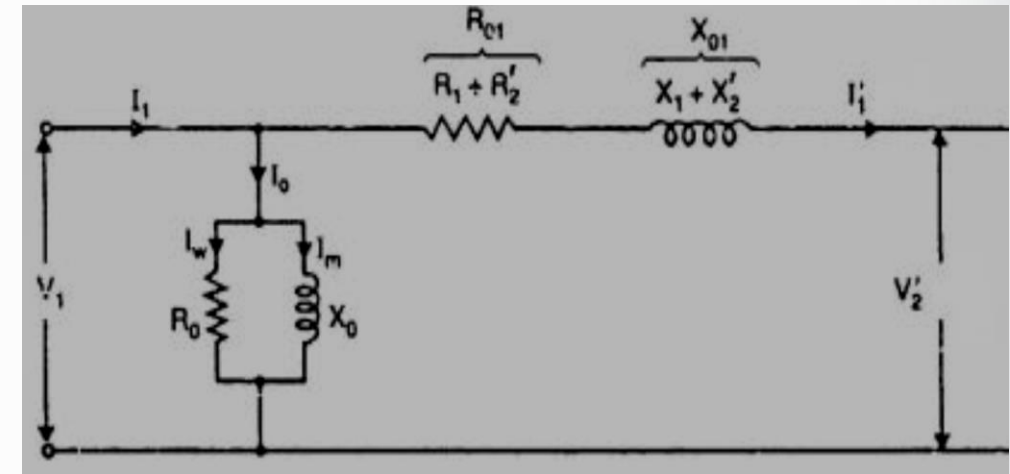
## Approximate Equivalent circuit referred to primary side:




$$R_2' = R_2 / K^2$$

$$X_2' = X_2 / K^2$$

$$V_2' = V_2 / K$$

$$I_2' = KI_2$$

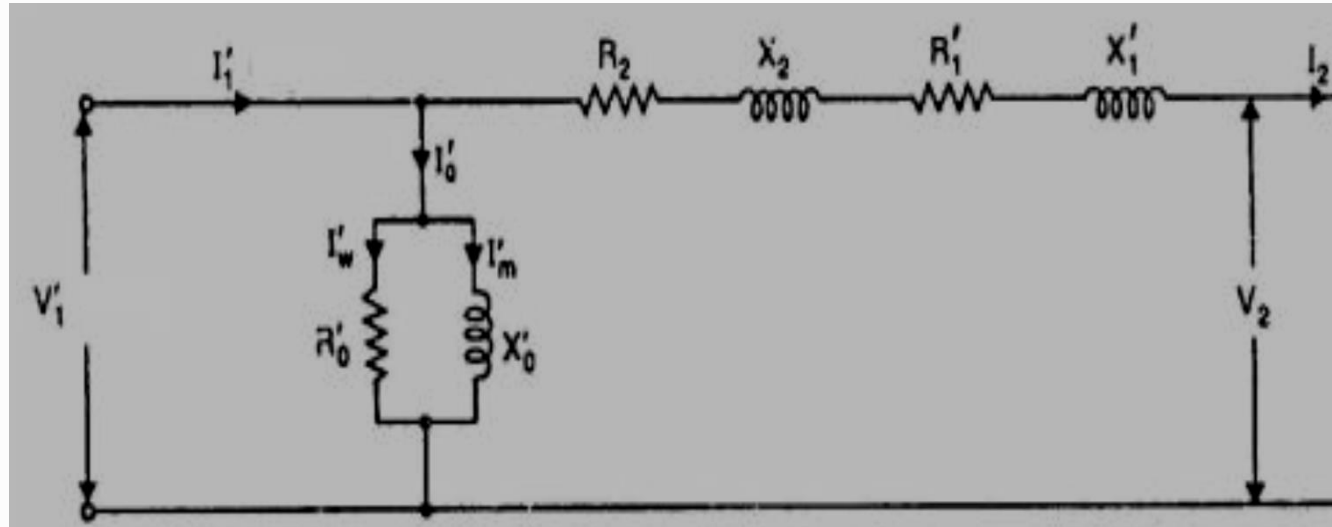

$$V_1' = V_1 K$$

$$I_1' = I_1 / K$$

# Transformer Tests




- The performance of a transformer can be calculated on the basis of equivalent circuit
- The four main parameters of equivalent circuit are:
  - $R_{01}$  as referred to primary (or secondary  $R_{02}$ )
  - the equivalent leakage reactance  $X_{01}$  as referred to primary (or secondary  $X_{02}$ )
  - Magnetising susceptance  $B_0$  (or reactance  $X_0$ )
  - core loss conductance  $G_0$  (or resistance  $R_0$ )
- The above constants can be determined by two tests
  - Open circuit test (O.C test / No load test)
  - Short circuit test (S.C test/Impedance test)
- These tests are economical and convenient
  - these tests furnish the result without actually loading the transformer
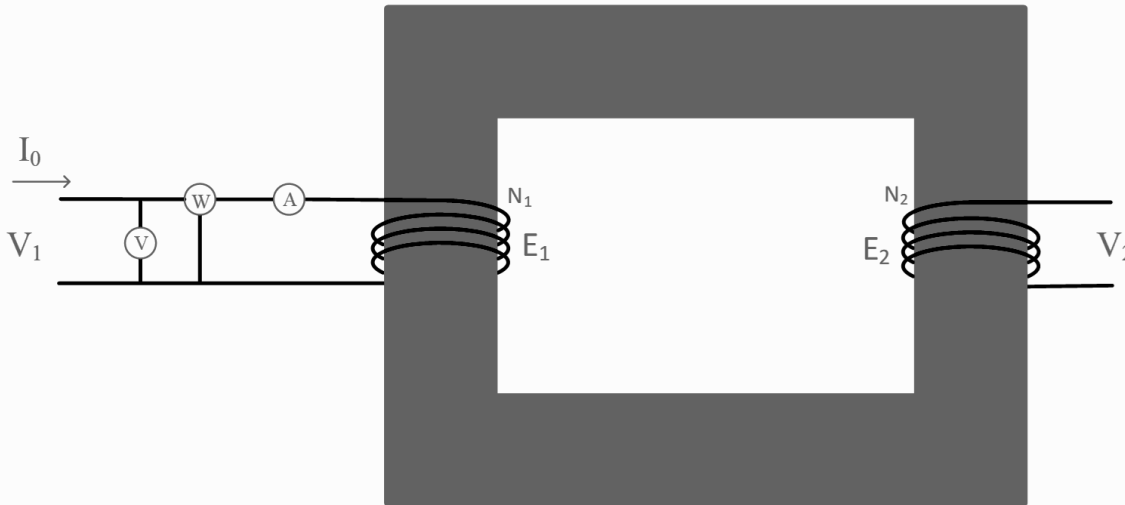
# Open-circuit Test



In Open Circuit Test the transformer's **secondary winding is open-circuited**, and its **primary winding is connected to a full-rated line voltage**.



- To find
  - (i) No load loss or core loss
  - (ii) No load current  $I_0$  which is helpful in finding  $G_o$  (or  $R_o$ ) and  $B_o$  (or  $X_o$ )

$$\text{Core loss} = W_{oc} = V_0 I_0 \cos \phi_0$$

$$\cos \phi_0 = \frac{W_{oc}}{V_0 I_0}$$

$$I_c \text{ or } I_w = I_0 \cos \phi_0$$

$$I_m \text{ or } I_\mu = I_0 \sin \phi_0 = \sqrt{I_0^2 - I_w^2}$$

$$I_0 = V_0 Y_0; \quad \therefore Y_0 = \frac{I_0}{V_0}$$

$$R_o = \frac{V_o}{I_w}$$

$$X_o = \frac{V_o}{I_m}$$



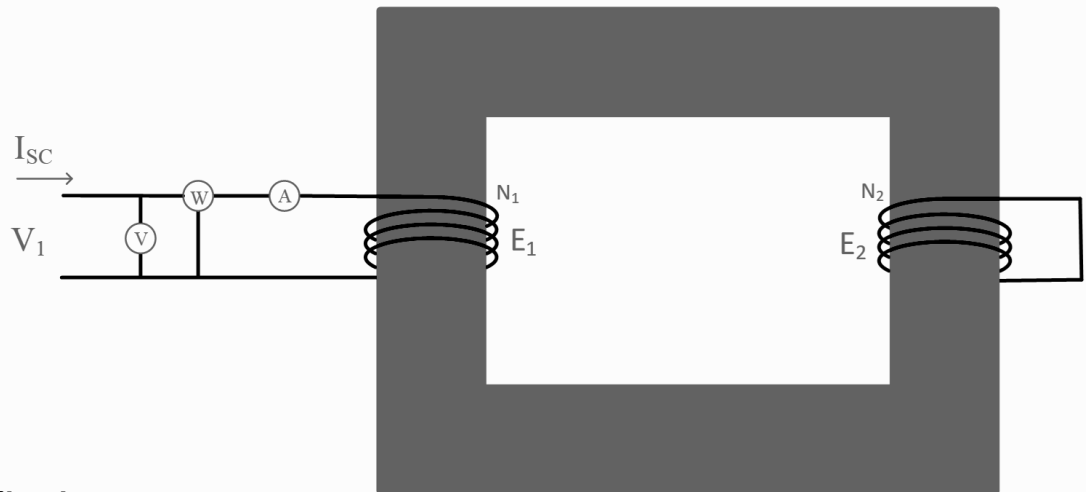
# Short-circuit Test



In Short Circuit Test the **secondary terminals are short circuited**, and the **primary terminals are connected to a fairly low-voltage source**.

The **input voltage is adjusted until the current in the short circuited windings is equal to its rated value**. The input voltage, current and power is measured.



- To find
  - (i) Full load copper loss – to pre determine the efficiency
  - (ii)  $Z_{01}$  or  $Z_{02}$ ;  $X_{01}$  or  $X_{02}$ ;  $R_{01}$  or  $R_{02}$  - to predetermine the voltage regulation

$$\text{Full load cu loss} = W_{sc} = I_{sc}^2 R_{01}$$

$$R_{01} = \frac{W_{sc}}{I_{sc}^2}$$

$$Z_{01} = \frac{V_{sc}}{I_{sc}}$$

$$\therefore X_{01} = \sqrt{Z_{01}^2 - R_{01}^2}$$

# Transformer Voltage Regulation

The output voltage of a transformer varies with the load even if the input voltage remains constant. This is because a real transformer has series impedance within it.

Voltage regulation is defined as the change in secondary terminal voltage when transformer state changes from no load to full load or vice versa, and the change in terminal voltage is expressed as percentage change with respect to the terminal voltage at the initial state of the transformer (no load voltage/full load voltage).


$$\% \text{ Voltage Regulation} = \frac{V_2[\text{no-load}] - V_2[\text{full-load}]}{V_2[\text{no-load}]} \times 100$$

$$\approx \frac{V_1[\text{no-load}] - V_1[\text{full-load}]}{V_1[\text{no-load}]} \times 100$$

—————> Referred to the primary side
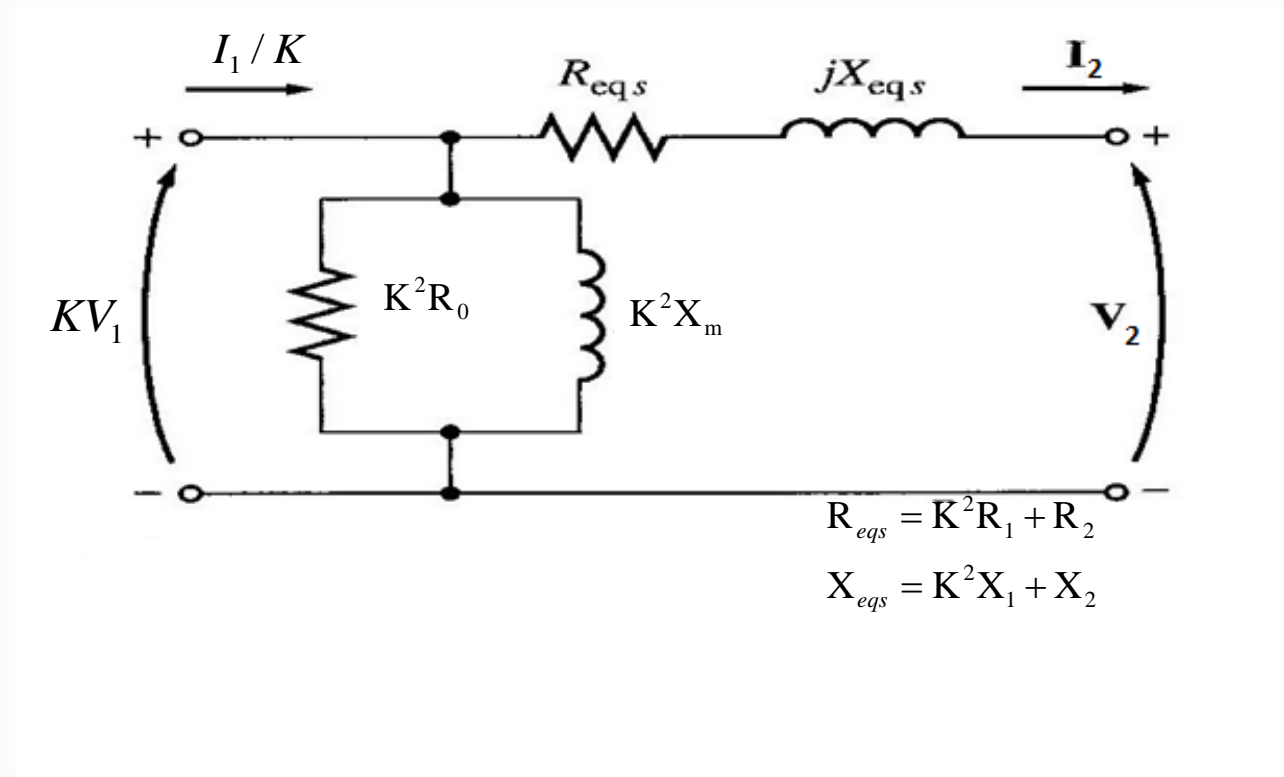
# Transformer Voltage Regulation

To determine the voltage regulation of a transformer, it is necessary to understand the voltage drops within it. Below is approximate equivalent circuit referred to secondary side



# Transformer Voltage Regulation

- Ignoring the excitation of the branch (since the current flow through the branch is considered to be small), more consideration is given to the series impedances ( $R_{eq} + jX_{eq}$ ).
- ***Voltage Regulation depends on magnitude of the series impedance and the phase angle of the current flowing through the transformer.***
- Phasor diagrams will determine the effects of these factors on the voltage regulation. A phasor diagram consist of current and voltage vectors.
- Assume that the reference phasor is the secondary voltage,  $V_2$ . Therefore the reference phasor will have 0 degrees in terms of angle.

***Based upon the equivalent circuit, apply Kirchoff Voltage Law***

$$KV_1 = V_2 + R_{eq}I_2 + jX_{eq}I_2$$

# Losses in a Transformer



- The power losses in a transformer are of two types:
  1. Core losses/Iron losses /Constant losses
  2. Copper losses/Variable losses

These losses appear in the form of heat and result in (i) increase in temperature and (ii) drop in efficiency
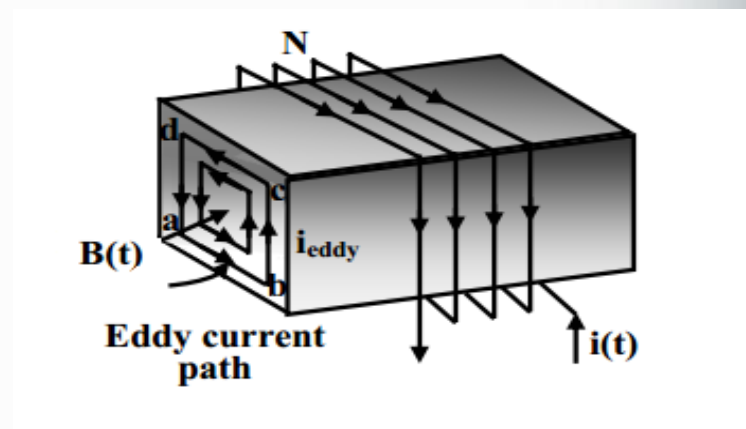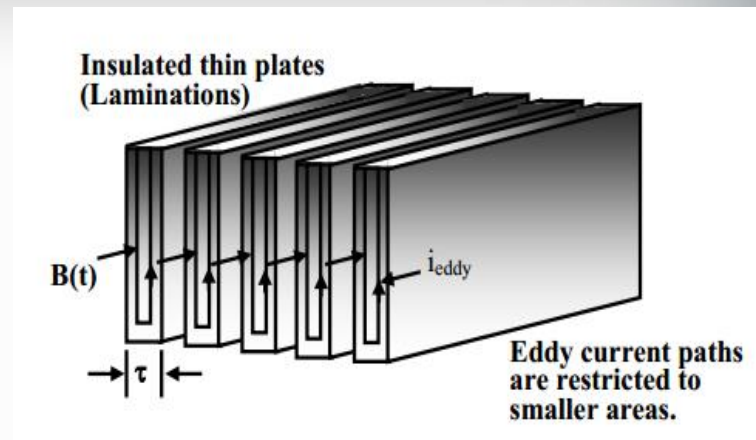
## (a) Core or Iron losses ( $P_i$ ):

These consist of hysteresis and eddy current losses and occur in the transformer core due to the alternating flux.

**Eddy current losses:** Eddy current losses are resistive heating losses in the core of the transformer. They are proportional to the square of the voltage applied to the transformer.





# Losses in a Transformer contd..



**Hysteresis losses:** Hysteresis losses are associated with the rearrangement of the magnetic domains in the core during each half-cycle. They are a complex, nonlinear function of the voltage applied to the transformer.



## (a) Iron or Core losses

$$P_i = \text{Hysteresis loss} + \text{Eddy current loss} = \text{Constant losses}$$
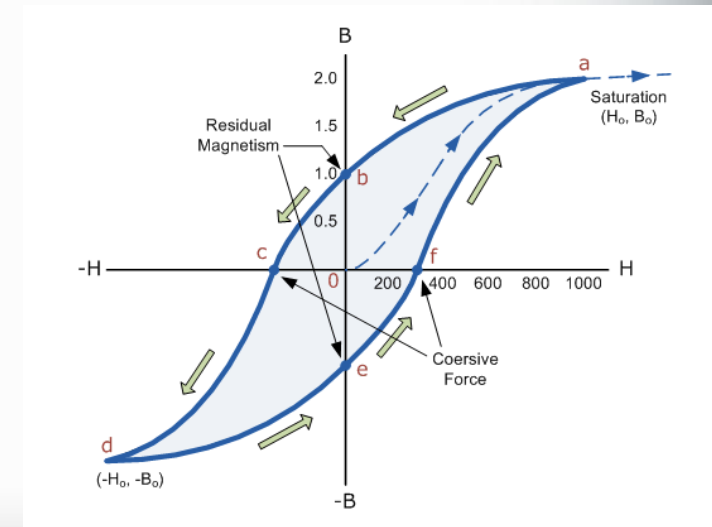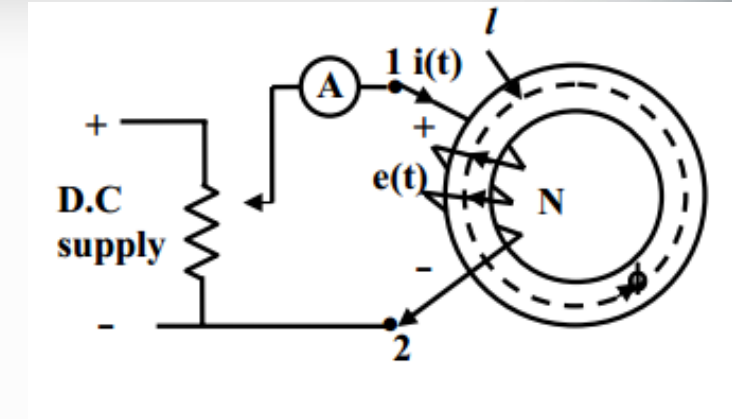
## • (b) Copper ( $I^2R$ ) losses

Copper losses are the resistive heating losses in the primary and secondary windings of the transformer. They are proportional to the square of the current in the windings.

$$\text{Total Cu losses, } P_c = I_1^2 R_1 + I_2^2 R_2 = I_1^2 R_{01} + I_2^2 R_{02}$$



# Transformer Efficiency

$$\eta = \frac{\text{Power Output}}{\text{Power Input}}$$

$$= \frac{\text{Power Input} - \text{Losses}}{\text{Power Input}}$$

$$= 1 - \frac{\text{Losses}}{\text{Power Input}}$$

$$= 1 - \frac{P_{\text{cu}} + P_{\text{core loss}}}{P_{\text{cu}} + P_{\text{core loss}} + V_2 I_2 \cos \theta}$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{out}} + P_{\text{loss}}} \times 100\%$$

$$\eta = \frac{V_2 I_2 \cos \theta}{P_{\text{cu}} + P_{\text{core}} + V_2 I_2 \cos \theta} \times 100\%$$

Usually the efficiency for a power transformer is between 0.9 to 0.99. The higher the rating of a transformer, the greater is its efficiency.

# Three Phase Transformers




➤ Three phase transformer can be formed by two ways:


- (a) Three identical single-phase transformers may be connected so that the three windings of one voltage (say primary) are connected in  $\Delta$  (or Y) and other three windings of the other voltage (secondary) are connected in Y (or  $\Delta$ ) to form a three phase transformer of different connections  $\Delta$ -Y, Y- $\Delta$ , Y-Y and  $\Delta$ - $\Delta$
- (b) All three phases are wound on the same core, as a single unit

Three phase bank	Single unit
Reliable. If one phase is faulty , we can repair it very easily	Less reliable. Entire unit needs to be repaired if one phase is faulty
If one phase is fault, it can be operated with the other two in open-delta connection	Can't supply power to load using two phases
Cost is more	Less cost compared to 3-phase bank, due to less iron requirement because of common core

# Three phase transformers

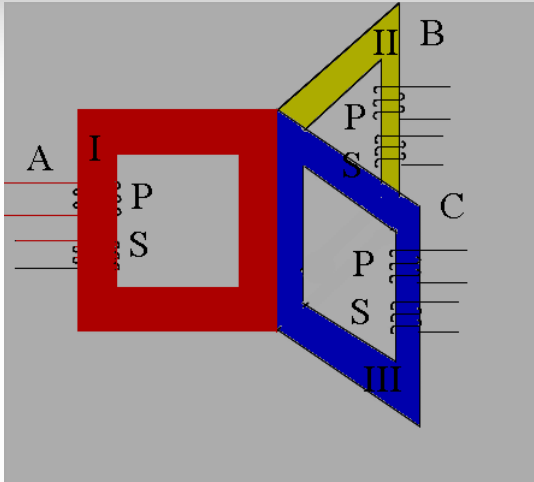

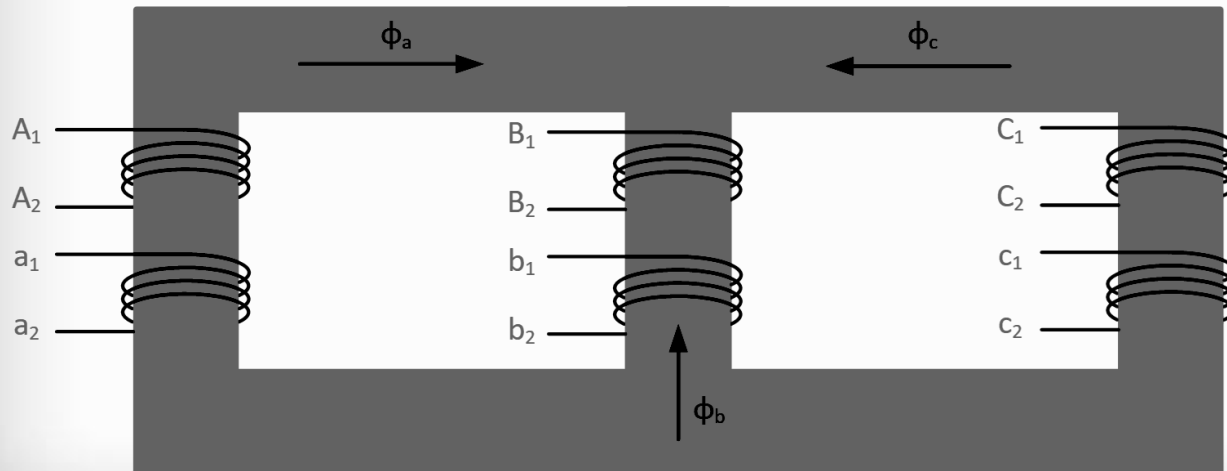3 $\phi$  transformer comprised of three single phase units is called transformer bank



Usually 3 $\phi$  transformers are constructed so all windings share a common core, i.e., as a single unit


# Three Phase Transformer Connections

- There are 4 different ways to connect 3 $\phi$  transformers


Connections	Line voltages	Phase displacement between primary and secondary
$\Delta$ - $\Delta$	$V_1 : V_1 / K$	$0^\circ$
Y-Y	$V_1 : V_1 / K$	$0^\circ$
$\Delta$ -Y	$V_1 : (\sqrt{3} * V_1) / K$	$30^\circ$
Y- $\Delta$	$V_1 : (V_1 / \sqrt{3}) * K$	$-30^\circ$




# Three Phase Transformer Connections

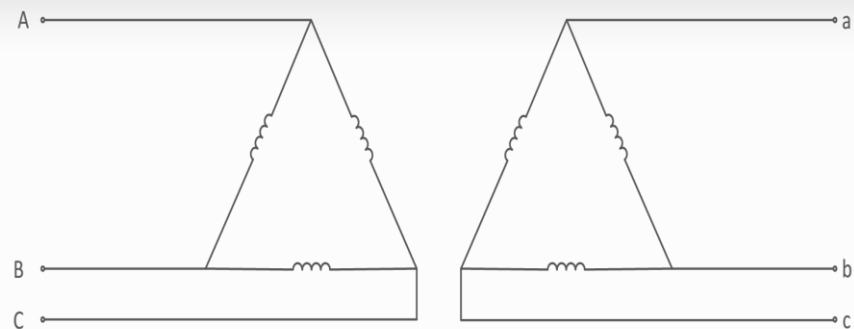

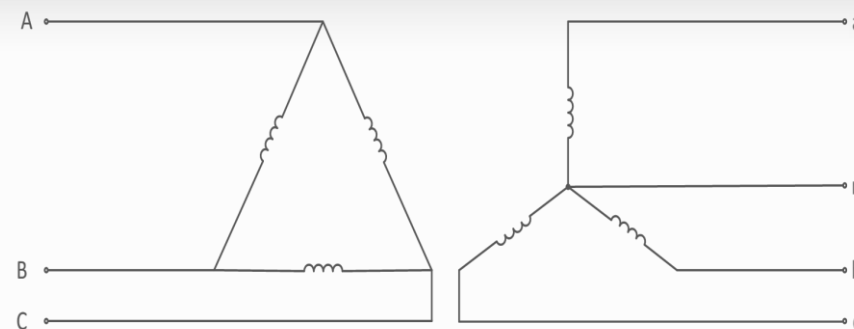
$\Delta/\Delta$  connection  
Phase shift =  $0^\circ$



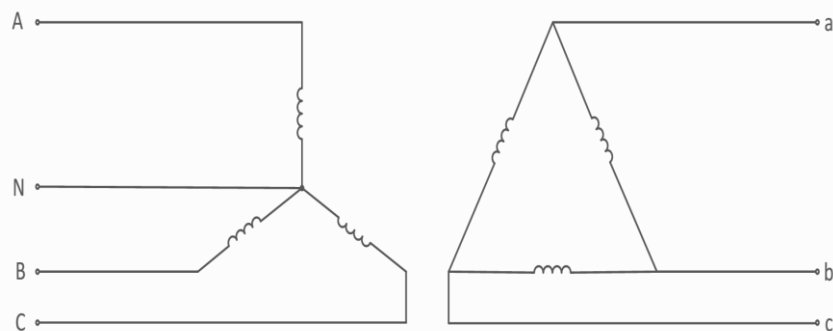$\Delta/Y$  connection  
Phase shift =  $30^\circ$



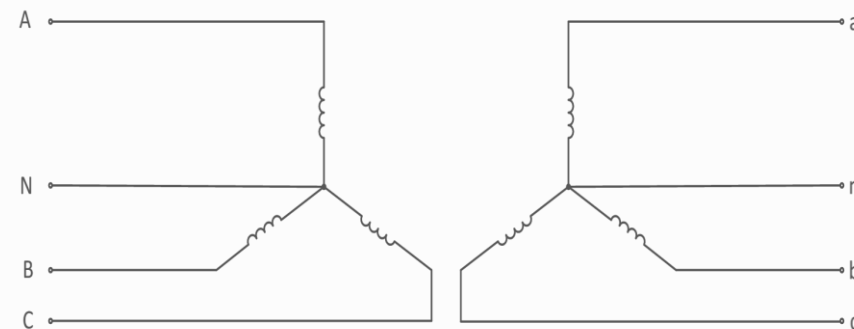
$Y/\Delta$  connection  
Phase shift =  $-30^\circ$




$Y/Y$  connection  
Phase shift =  $0^\circ$

# Three Phase Transformer Connections

## Y-Y connection

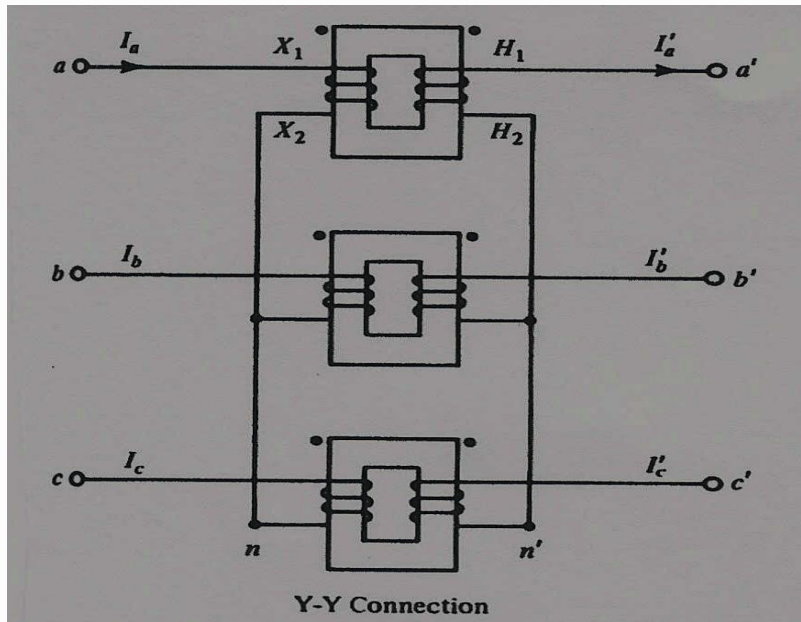


## $\Delta$ - $\Delta$ connection

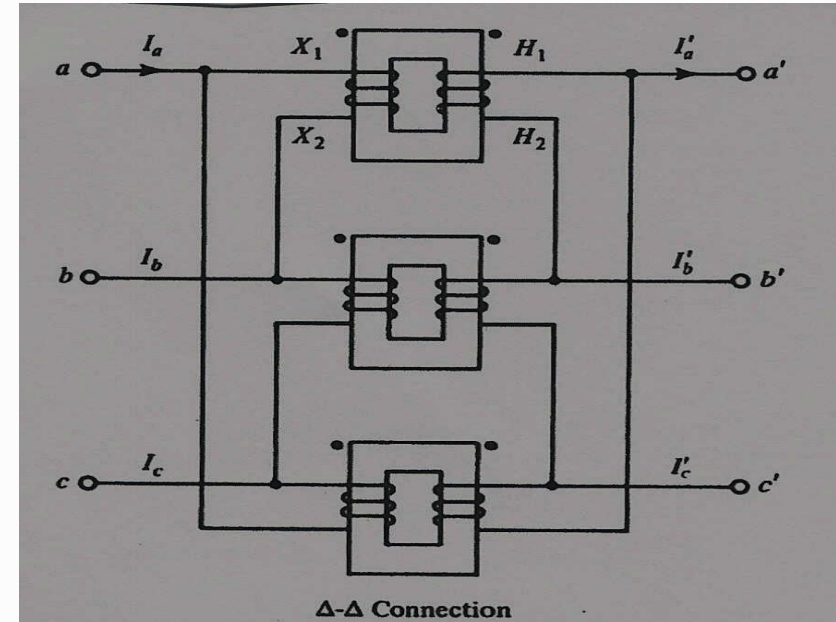


# Three Phase Transformer Connections

## $\Delta$ -Y connection

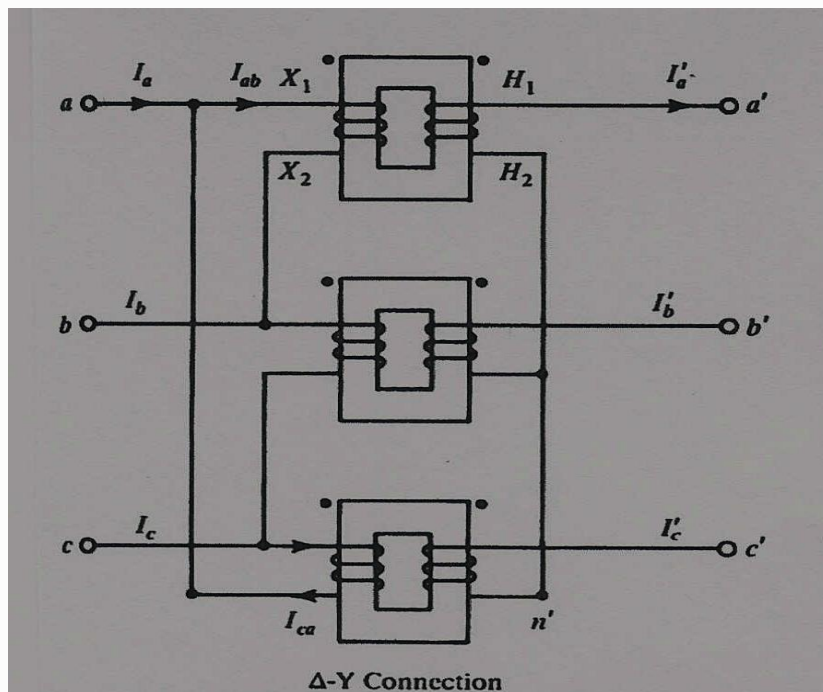

## Y- $\Delta$ connection

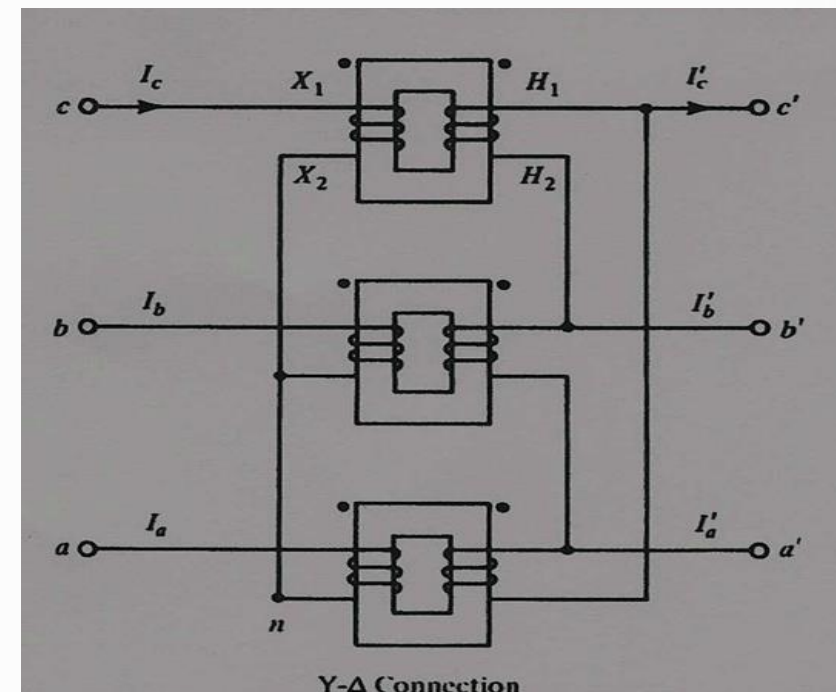



# Detailed 3-phase model

