

EN304- ELECTRICAL ENERGY SYSTEMS



Department of Energy Science and Engineering


This is only reading material (not lecture slides)

Cl: Zakir H Rather

Note: Some contents of the reading material presented in the supporting slides are gleaned from different resources for which the copyright is retained by the respective owner/holder/creator/publisher. The instructor of EN 209 does not hold any copyrights to the material obtained from such various resources. You are advised to treat the supporting slides as education material and not to exchange, disseminate, or share them with any other entity.




SLIDE DECK 1: THREE PHASE CIRCUITS

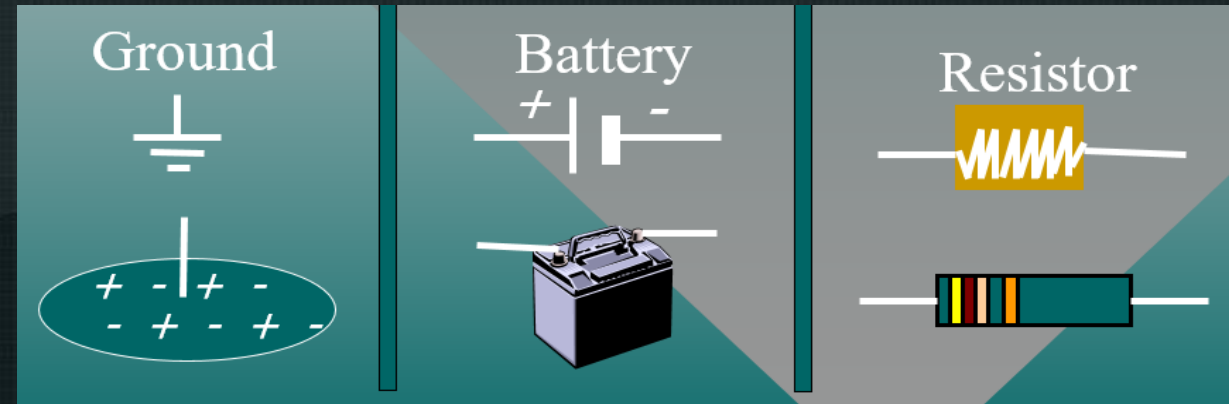


Concept of three phase system



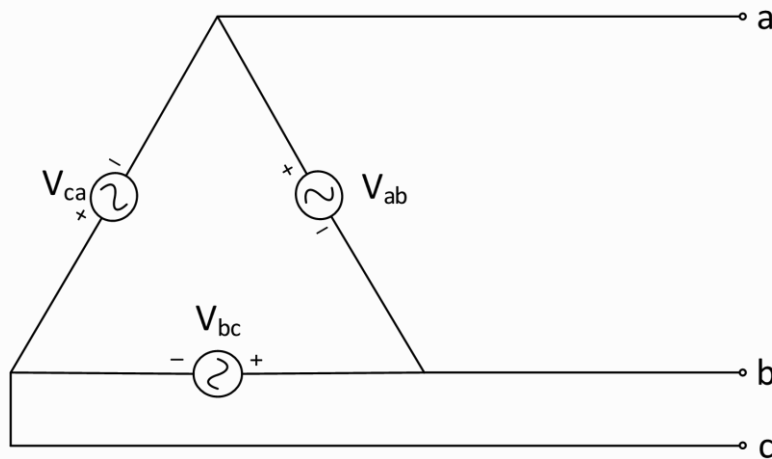A typical three-phase system consists of three voltage sources connected to loads by three or four wires (or transmission lines). A three-phase system is equivalent to three single-phase circuits. The voltage sources can be either wye-connected or delta-connected as shown in the figure.



Delta-connected source

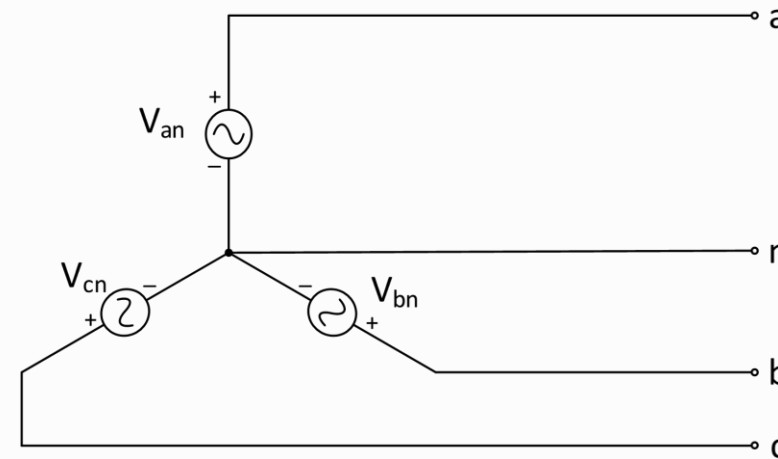

wye-connected source

Where v_{an} , v_{bn} and v_{cn} are respectively the voltage differences between the phases a, b, c and neutral n. and they are called phase voltages.

Concept of 3 ϕ system

Y-connected source

Phase sequence

Line & phase voltages in Y-connected sys.

Line & phase currents in Δ -connected sys.

Power in 3 ϕ system

Why 3 ϕ system?

Concept of three phase system (wye connected source)



- Balanced phase voltages are equal in magnitude and are out of phase with each other by 120° .
- Note that for balanced phase voltages the following equations are valid:

$$\begin{aligned}v_{an} + v_{bn} + v_{cn} &= 0 \\|v_{an}| &= |v_{bn}| = |v_{cn}|\end{aligned}$$

- For balanced phase voltage, assuming $|V_{an}| = |V_{bn}| = |V_{cn}| = V_P$, we can write the following phasors of phase voltages,



$$V_{an} = V_P \angle 0^\circ$$

$$V_{bn} = V_P \angle -120^\circ$$

$$V_{cn} = V_P \angle -240^\circ = V_P \angle +120^\circ$$

See the phasor diagram and notice that the positive direction is counter clockwise direction.

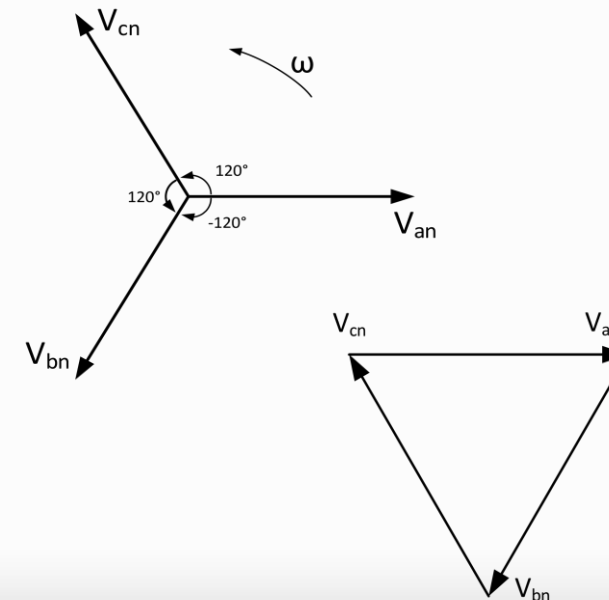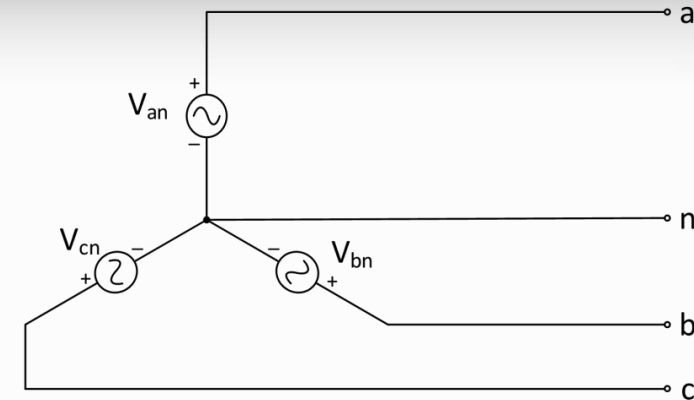- Notice that the 120° phase difference between the phases is the reason of $v_{an} + v_{bn} + v_{cn} = 0$. (prove it mathematically)



Concept of 3 ϕ system

Y-connected source

Phase sequence

Line & phase voltages in Y-connected sys.

Line & phase currents in Δ -connected sys.


Power in 3 ϕ system

Why 3 ϕ system?

Phase sequence in three phase system

- The phase sequence is the time order in which the voltages pass through their respective maximum values.
- The phase sequence is determined by the order in which the phasors pass through a fixed point in the phasor diagram. abc sequence is called positive sequence and acb sequence is called negative sequence. See the following phasors, mathematical representations and waveforms for both sequences.

Positive sequence

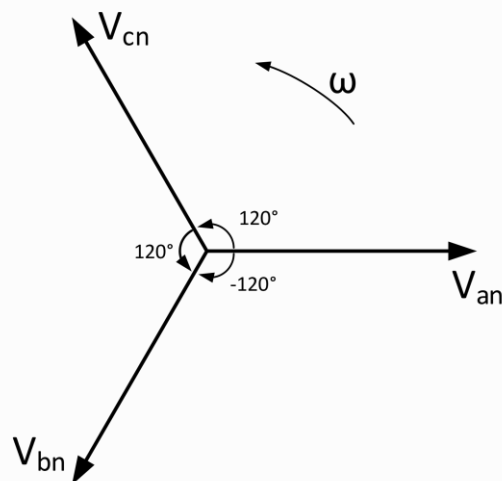


$$V_{an} = V_P \angle 0^\circ$$

$$V_{bn} = V_P \angle -120^\circ$$

$$V_{cn} = V_P \angle -240^\circ = V_P \angle +120^\circ$$

Negative sequence

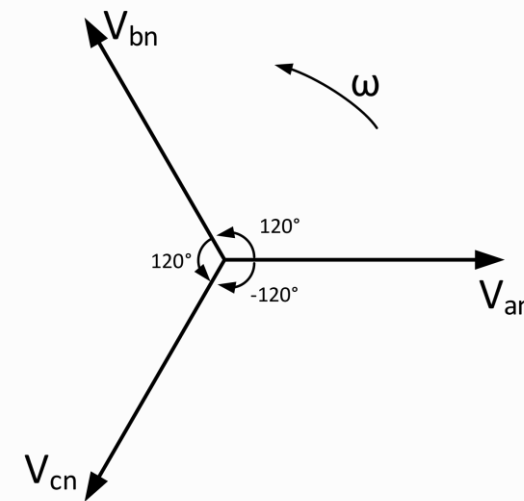

$$V_{an} = V_P \angle 0^\circ$$

$$V_{cn} = V_P \angle -120^\circ$$

$$V_{bn} = V_P \angle -240^\circ = V_P \angle +120^\circ$$

Concept of 3 ϕ system

Y-connected source

Phase sequence

Line & phase voltages in Y-connected sys.

Line & phase currents in Δ -connected sys.


Power in 3 ϕ system

Why 3 ϕ system?

Phase sequence in three phase system




Positive sequence

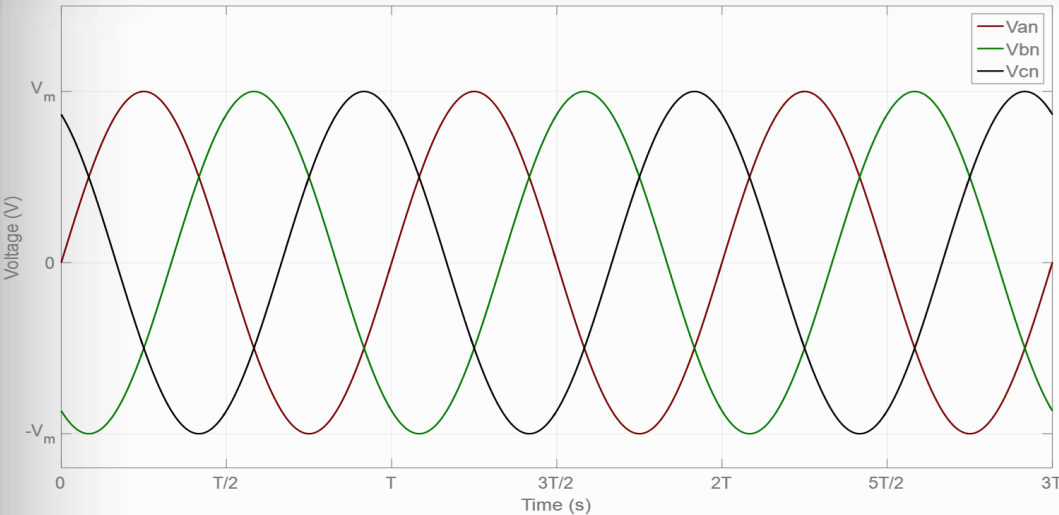


$$\begin{aligned} v_{an}(t) &= V_{an} \sin(\omega t) \\ v_{bn}(t) &= V_{bn} \sin(\omega t - 120^\circ) \\ v_{cn}(t) &= V_{cn} \sin(\omega t - 240^\circ) \end{aligned}$$

OR
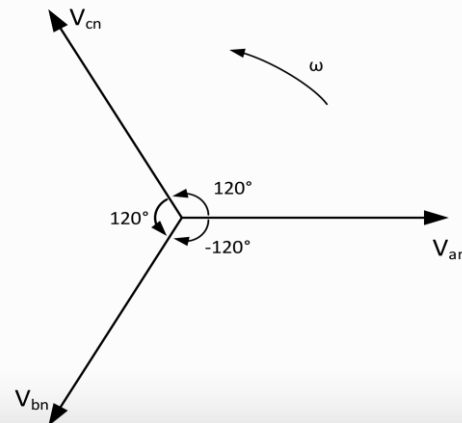
$$\begin{aligned} v_{an}(t) &= V_{an} \sin(\omega t) \\ v_{bn}(t) &= V_{bn} \sin(\omega t + 240^\circ) \\ v_{cn}(t) &= V_{cn} \sin(\omega t + 120^\circ) \end{aligned}$$




Negative sequence

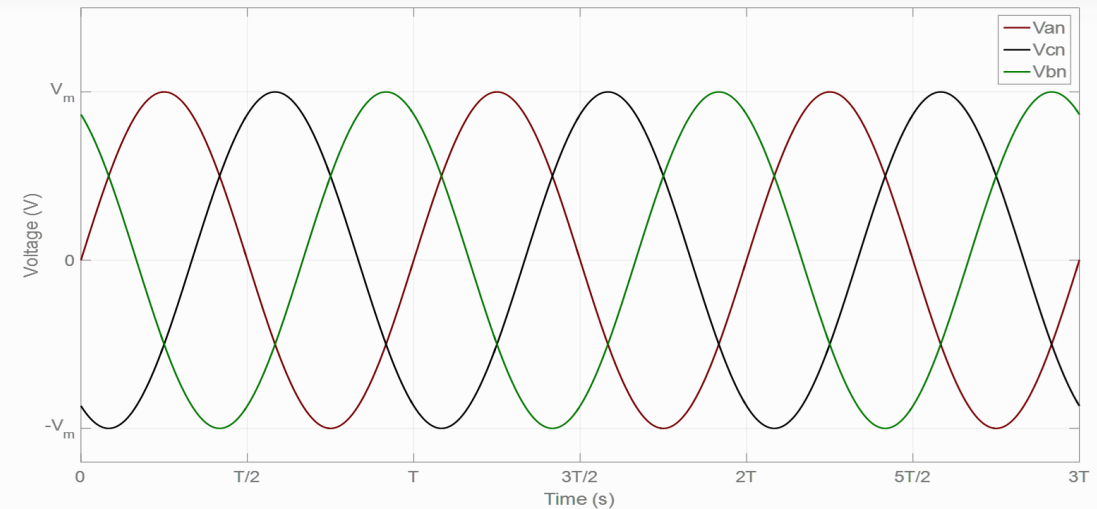

$$\begin{aligned} v_{an}(t) &= V_{an} \sin(\omega t) \\ v_{bn}(t) &= V_{bn} \sin(\omega t + 120^\circ) \\ v_{cn}(t) &= V_{cn} \sin(\omega t + 240^\circ) \end{aligned}$$

OR
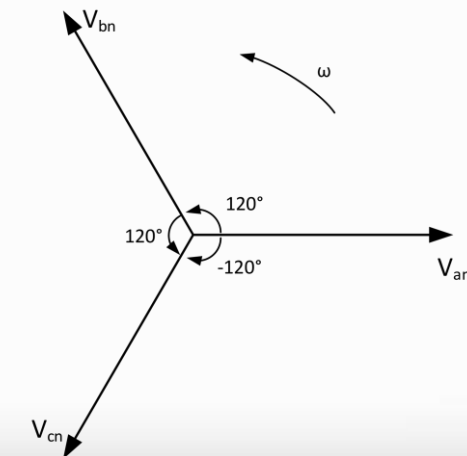
$$\begin{aligned} v_{an}(t) &= V_{an} \sin(\omega t) \\ v_{bn}(t) &= V_{bn} \sin(\omega t - 240^\circ) \\ v_{cn}(t) &= V_{cn} \sin(\omega t - 120^\circ) \end{aligned}$$



Concept of 3 ϕ system

Y-connected source

Phase sequence

Line & phase voltages in Y-connected sys.

Line & phase currents in Δ -connected sys.

Power in 3 ϕ system

Why 3 ϕ system?

Line voltage and phase voltage in balanced system (wye connected source)



- The voltage difference between any two lines is called line voltage (V_{ab}, V_{bc}, V_{ca}). These line voltages are related to phase voltages.



$$V_{ab} = V_{an} - V_{bn} = V_P \angle 0^\circ - V_P \angle -120^\circ = \sqrt{3}V_P \angle 30^\circ$$

Similarly,

$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3}V_P \angle -90^\circ$$

$$V_{ca} = V_{cn} - V_{an} = \sqrt{3}V_P \angle -210^\circ$$

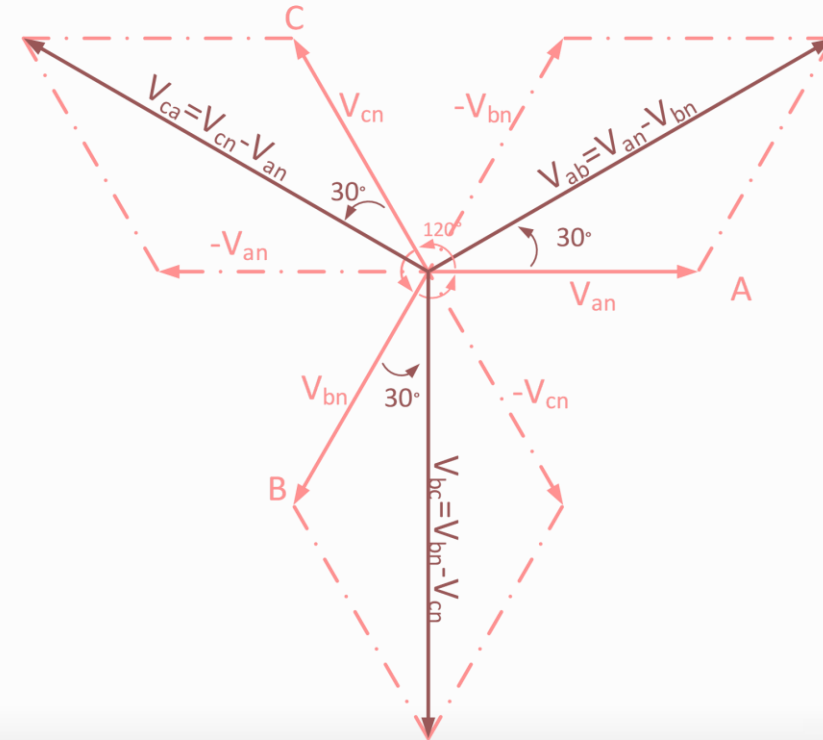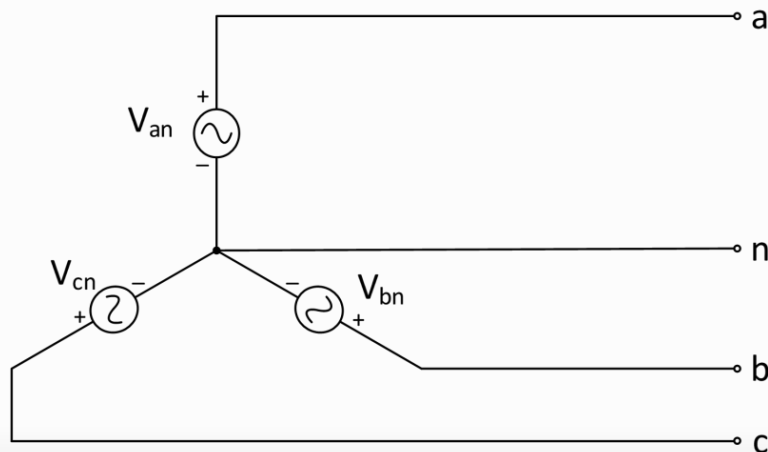See the phasor diagram of phase and line voltage.



Concept of 3 ϕ system

Y-connected source

Phase sequence

Line & phase voltages in Y-connected sys.

Line & phase currents in Δ -connected sys.

Power in 3 ϕ system

Why 3 ϕ system?

Line voltage and phase voltage in balanced system (wye connected source)

- Notice that in balanced voltage system: $|V_{ab}| = |V_{bc}| = |V_{ca}| = |V_L| = \sqrt{3} |V_P|$
 $|V_{an}| = |V_{bn}| = |V_{cn}| = |V_P|$

where V_L is the line voltage.

- When a balanced wye-connected source is loaded by balanced load, the phase currents are balanced as well. If I_a is taken as reference, then

$$I_b = I_a \angle -120^\circ$$


$$I_c = I_a \angle -240^\circ$$

The neutral current is calculated by applying KCL,

$$I_n = I_a + I_b + I_c = 0$$

Hence, when a balanced wye-connected source is loaded by balanced load, the neutral current is zero
 And the neutral voltage is zero as well.

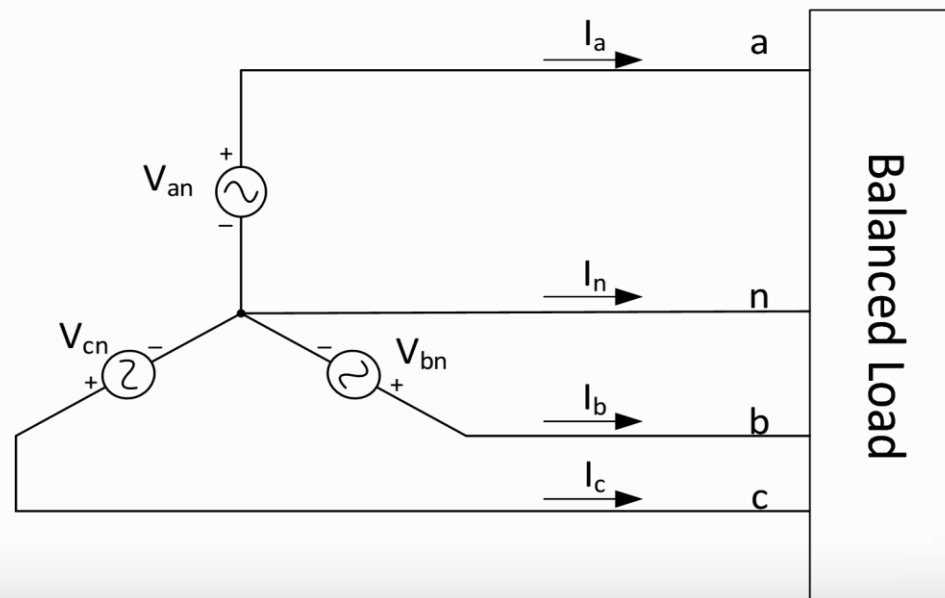- Note that in wye-connected systems line currents
 And phase currents are equal.



Concept of 3 ϕ system

Y-connected source

Phase sequence

Line & phase voltages in Y-connected sys.

Line & phase currents in Δ -connected sys.

Power in 3 ϕ system

Why 3 ϕ system?

Three phase balanced system (delta connected source)





- In delta connected system, neutral does not exist.
- I_{ab} , I_{bc} and I_{ca} are the phase currents. I_a , I_b and I_c are the line currents. Assuming that source and the load are balanced, the phase currents can be written as follows,

$$I_{ab} = I_P \angle 0^\circ$$

$$I_{bc} = I_P \angle -120^\circ$$

$$I_{ca} = I_P \angle -240^\circ$$

Where I_P is the phase current.

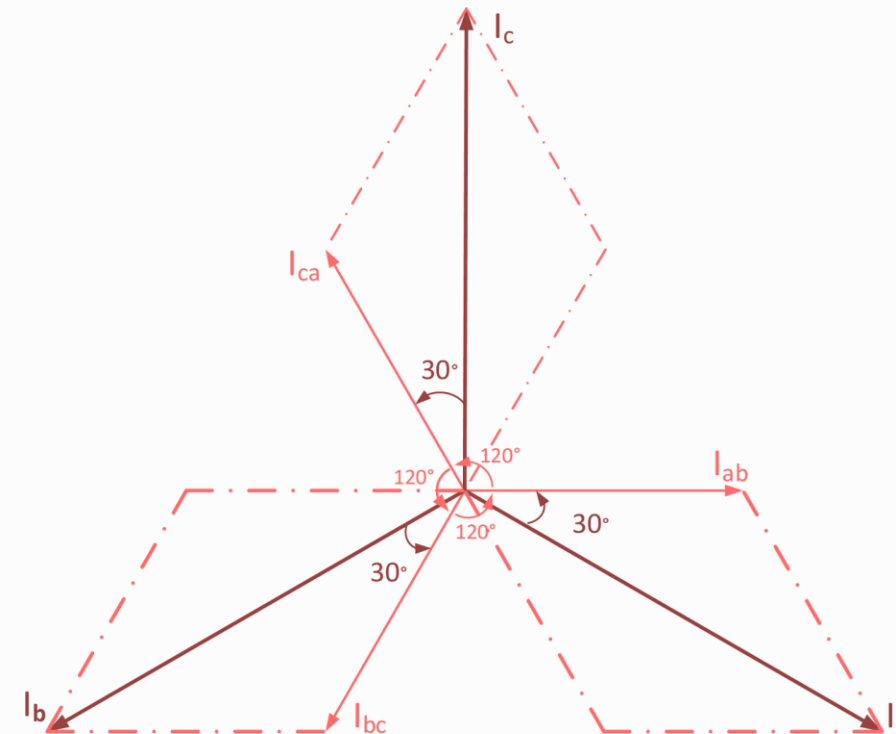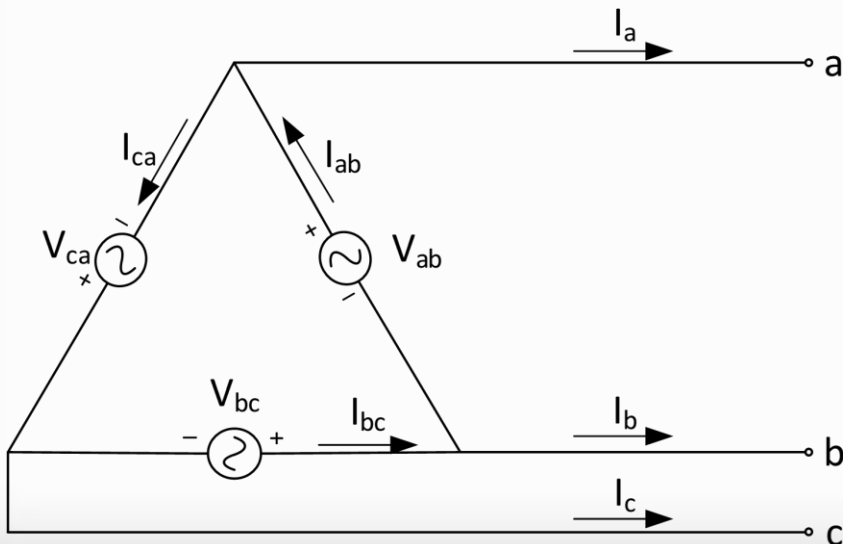

Concept of 3 ϕ
system

Y-connected
source

Phase
sequence

Line & phase
voltages in Y-
connected sys.

Line & phase
currents in Δ -
connected sys.

Power in 3 ϕ
system

Why
3 ϕ system?

Three phase balanced system (delta connected source)

- Applying KCL at the nodes a, b and c we get,



$$I_a = I_{ab} - I_{ca} = I_P \angle 0^\circ - I_P \angle -240^\circ = \sqrt{3} I_P \angle -30^\circ$$

Similarly,

$$I_b = I_{bc} - I_{ab} = \sqrt{3} I_P \angle -150^\circ$$

$$I_c = I_{ca} - I_{bc} = \sqrt{3} I_P \angle -270^\circ$$

- Notice that $|I_a| = |I_b| = |I_c| = I_L$ and $|I_{ab}| = |I_{bc}| = |I_{ca}| = I_P$
where $I_L = \sqrt{3} I_P$

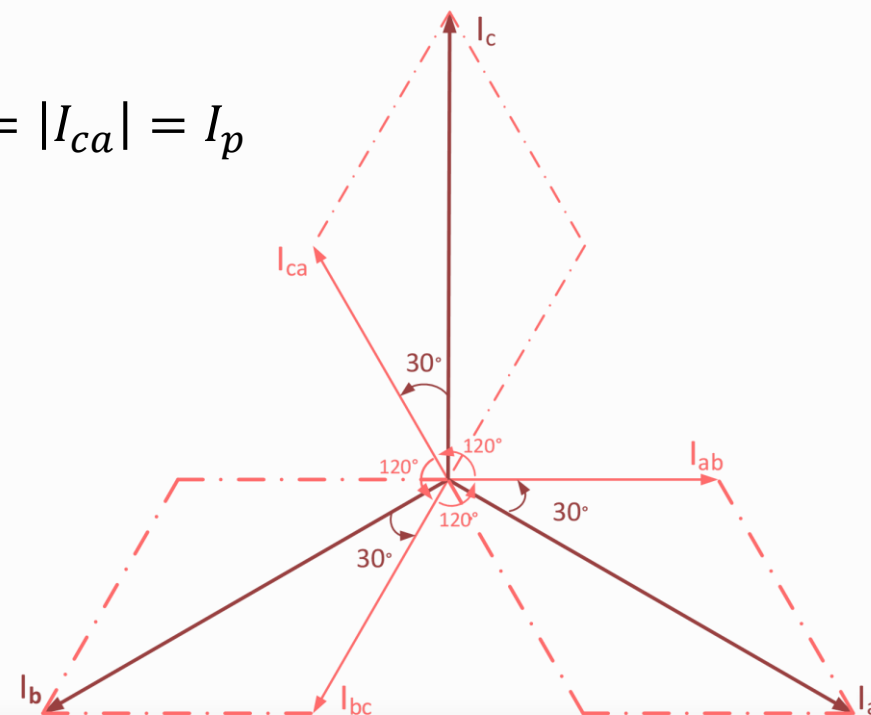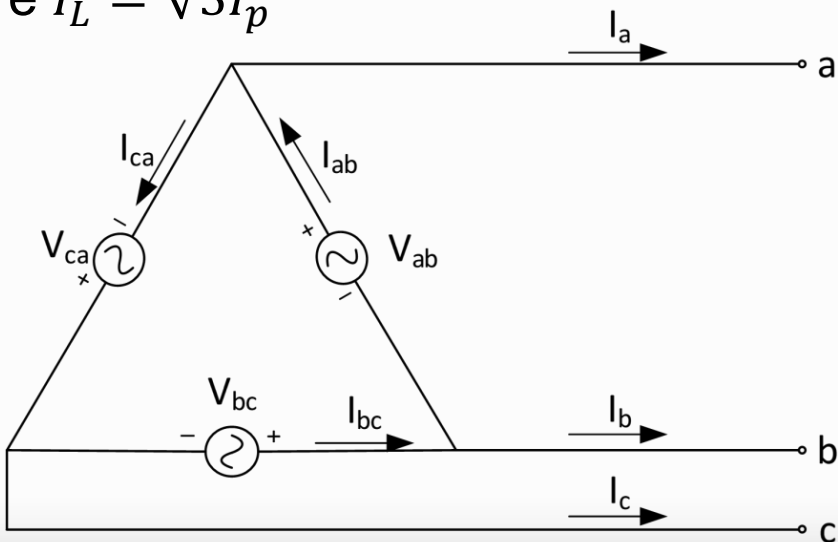

Concept of 3 ϕ system

Y-connected source

Phase sequence

Line & phase voltages in Y-connected sys.

Line & phase currents in Δ -connected sys.

Power in 3 ϕ system

Why 3 ϕ system?

Power in balanced three phase system



- For a Y-connected load, the phase voltages are given by,

$$v_{an}(t) = \sqrt{2}v_P \sin(\omega t)$$

$$v_{bn}(t) = \sqrt{2}v_P \sin(\omega t - 120^\circ)$$

$$v_{cn}(t) = \sqrt{2}v_P \sin(\omega t - 240^\circ)$$

- If the load impedance is $Z_Y = Z \angle \theta$, then the phase currents lag their corresponding voltages by θ as follow,

$$i_a(t) = I \sin(\omega t - \theta)$$

$$i_b(t) = I \sin(\omega t - \theta - 120^\circ)$$

$$i_c(t) = I \sin(\omega t - \theta - 240^\circ)$$

$$\text{Where } I = \frac{\sqrt{2}v_P}{Z}$$

Concept of 3 ϕ system

Y-connected source

Phase sequence

Line & phase voltages in Y-connected sys.

Line & phase currents in Δ -connected sys.

Power in 3 ϕ system

Why 3 ϕ system?

Power in balanced three phase system



- The total instantaneous power in the load is the sum of the instantaneous powers in the three phases,

$$P = P_a + P_b + P_c = v_{an}i_a + v_{bn}i_b + v_{cn}i_c \implies P = 3v_P i_P \cos(\theta) = \sqrt{3} v_L i_L \cos(\theta) \quad (*)$$

- Similarly, reactive power and complex power can be calculated as follows,

$$Q = 3v_P i_P \sin(\theta) = \sqrt{3} v_L i_L \sin(\theta) \quad S = 3v_P i_P^*$$

- Note that these equations apply for both Y-connected and Delta-connected loads.

Concept of 3 ϕ system

Y-connected source

Phase sequence

Line & phase voltages in Y-connected sys.

Line & phase currents in Δ -connected sys.

Power in 3 ϕ system

Why 3 ϕ system?